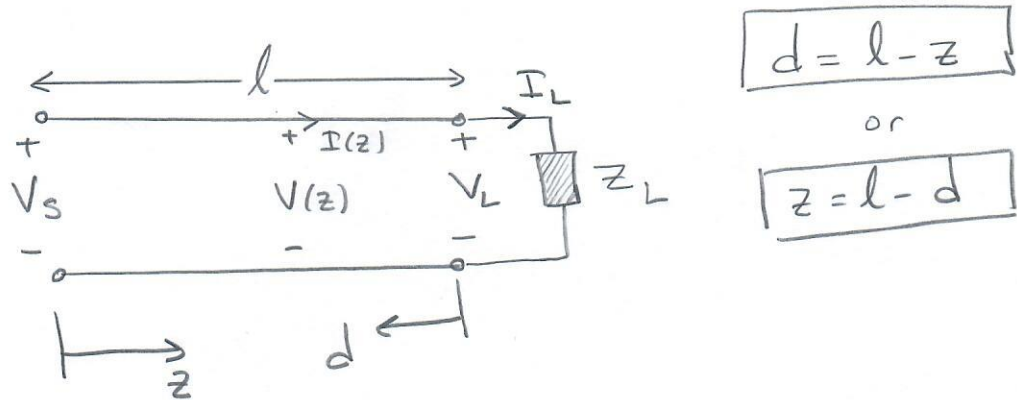


## REFLECTION COEFFICIENT in Transmission Lines

Consider a transmission line of length  $l$ .



$$V(z) = V^+ e^{-\gamma z} + V^- e^{+\gamma z} \quad \text{as found earlier.}$$

$$\boxed{V_s = V(z=0) = V^+ + V^-} \quad \text{at the source end}$$

$$V_L = V(z=l) = \underbrace{V^+ e^{-\gamma l}}_{\text{call } V_L^+} + \underbrace{V^- e^{+\gamma l}}_{\text{call } V_L^-}$$

$$\boxed{V_L = V_L^+ + V_L^-}$$

Similarly,

$$\boxed{I_L = I_L^+ + I_L^- = \frac{V_L^+}{Z_0} - \frac{V_L^-}{Z_0}}$$

$$\left. \begin{array}{l} \boxed{\frac{V_L}{I_L} = Z_L} \\ \text{at the} \\ \text{load end.} \end{array} \right\}$$

Now, define the reflection coefficient  $\Gamma_L$  at the load:

$$\boxed{\Gamma_L \triangleq \frac{V_L^-}{V_L^+}} = \frac{\text{Value of backward traveling voltage at load end}}{\text{Value of forward traveling voltage at load end}}$$

$$\text{Use } Z_L = \frac{V_L}{I_L} = \frac{V_L^+ + V_L^-}{\frac{1}{Z_0}(V_L^+ - V_L^-)} = Z_0 \frac{1 + \frac{V_L^-}{V_L^+}}{1 - \frac{V_L^-}{V_L^+}} \quad \left( \begin{array}{l} \text{divide both} \\ \text{num. and} \\ \text{denom. by} \\ V_L^+ \end{array} \right)$$

$$\Rightarrow \boxed{Z_L = Z_0 \frac{1 + \Gamma_L}{1 - \Gamma_L}} \quad \text{where } \Gamma_L \text{ is complex, in general.}$$

or solve for  $\Gamma_L$  in terms of  $Z_L$ :

$$\boxed{\Gamma_L = \frac{Z_L - Z_0}{Z_L + Z_0} = |\Gamma_L| e^{j\theta_L}} \quad \begin{array}{l} \text{reflection} \\ \text{coefficient} \\ \text{at the load} \end{array}$$

Now, let's obtain the reflection coefficient expression at an arbitrary location over the transmission line. Use the d-axis (measured from the load end) where  $d = l - z$ .

$$V(d) = V(z) \Big|_{z=l-d} = V^+ e^{-\gamma(l-d)} + V^- e^{\gamma(l-d)}$$

$$V(d) = \underbrace{V^+ e^{-\gamma l}}_{V_L^+} e^{\gamma d} + \underbrace{V^- e^{\gamma l}}_{V_L^-} e^{-\gamma d}$$

(Note that  $V_L^+$  and  $V_L^-$  are constants)

$$V(d) = \underbrace{V_L^+ e^{\gamma d}}_{\text{forward prop. wave}} + \underbrace{V_L^- e^{-\gamma d}}_{\text{backward prop. wave}}$$

Similarly,

$$\begin{aligned} I(d) &= I_L^+ e^{\gamma d} + I_L^- e^{-\gamma d} \\ &= \frac{V_L^+}{Z_0} e^{\gamma d} - \frac{V_L^-}{Z_0} e^{-\gamma d} \end{aligned}$$

$$I(d) = \frac{1}{Z_0} (V_L^+ e^{\gamma d} - V_L^- e^{-\gamma d})$$

\* The reflection coefficient  $\Gamma(d)$  at a distance "d" measured from the load is defined as

$$\Gamma(d) = \left. \frac{\text{backward trav. voltage}}{\text{forward trav. voltage}} \right|_{\text{at } d} = \frac{V_L^- e^{-\gamma d}}{V_L^+ e^{+\gamma d}}$$

$$\Gamma(d) = \frac{V_L^-}{V_L^+} e^{-2\gamma d}$$

where  $\frac{V_L^-}{V_L^+} = \Gamma_L$  (ref. coeff. at load)


$$\Rightarrow \Gamma(d) = \Gamma_L e^{-2\gamma d}$$

where  $\begin{cases} \gamma = \alpha + j\beta \text{ (prop. coeff.)} \\ \text{and} \\ \Gamma_L = |\Gamma_L| e^{j\theta_L} \end{cases}$

Therefore,

$$\Gamma(d) = |\Gamma_L| e^{-2\alpha d} e^{j(\theta_L - 2\beta d)}$$

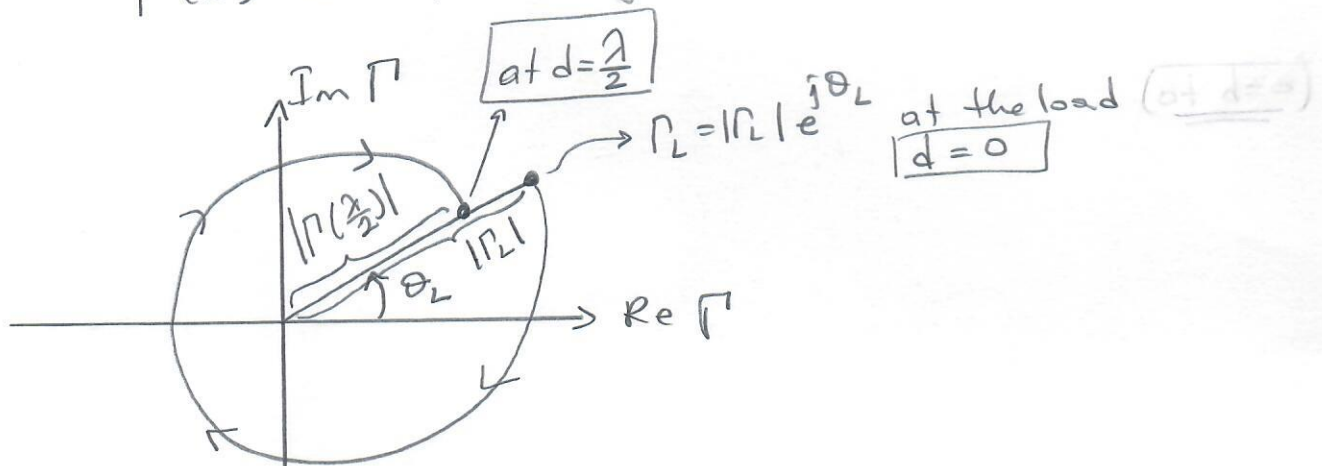$\Gamma(d)$  is complex in general,  $\Gamma(d) = \text{Re } \Gamma + j \text{Im } \Gamma$



$\Gamma$ -plane  
(Spiral locus for a lossy T.L.  $\alpha \neq 0$ )

(Note that for a lossless TL (with  $\alpha=0$ ), the tip of  $\Gamma(d)$  traces a circle)

At the load location (where  $d=0$ )  $\Gamma(d=0) = \Gamma_L = |\Gamma_L| e^{j\theta_L}$

Note that moving towards the source by  $d = \frac{\lambda}{2}$  corresponds to making a complete rotation in the  $\Gamma$ -plane, because:

We need  $2\beta d = 2\pi$  for a full cycle, where  $\boxed{\beta = \frac{2\pi}{\lambda}}$

$$2 \frac{2\pi}{\lambda} d = 2\pi$$

$$\Rightarrow \boxed{d = \frac{\lambda}{2}}$$

In a lossy T.L., due to  $\alpha \neq 0$ ,

$$|\Gamma(d)| = |\Gamma_L| e^{-2\alpha d}$$

i.e.  $|\Gamma(d)| < |\Gamma_L| \Rightarrow$  spiral locus of  $\Gamma(d)$  if  $\alpha \neq 0$ .



## IMPEDANCE of a Transmission Line, $Z(d)$

At a distance "d" measured from the load end, the impedance of the T.L. is defined as

$$Z(d) \triangleq \frac{V(d)}{I(d)} = \frac{V_L^+ e^{\gamma d} + V_L^- e^{-\gamma d}}{\frac{1}{Z_0} (V_L^+ e^{\gamma d} - V_L^- e^{-\gamma d})} \quad \left( \begin{array}{l} \text{divide both} \\ \text{num. and denom.} \\ \text{by } V_L^+ \end{array} \right)$$

$$= Z_0 \frac{e^{\gamma d} + \frac{V_L^-}{V_L^+} e^{-\gamma d}}{e^{\gamma d} - \frac{V_L^-}{V_L^+} e^{-\gamma d}} = Z_0 \frac{e^{\gamma d} + \Gamma_L e^{-\gamma d}}{e^{\gamma d} - \Gamma_L e^{-\gamma d}}$$

$$\left( \text{Remember } \frac{V_L^-}{V_L^+} \triangleq \Gamma_L = \frac{Z_L - Z_0}{Z_L + Z_0} \right)$$

$$\Rightarrow Z(d) = Z_0 \frac{e^{\gamma d} + \frac{Z_L - Z_0}{Z_L + Z_0} e^{-\gamma d}}{e^{\gamma d} - \frac{Z_L - Z_0}{Z_L + Z_0} e^{-\gamma d}} \quad \left( \begin{array}{l} \text{multiply both} \\ \text{num. and denom.} \\ \text{by } (Z_L + Z_0) \end{array} \right)$$

$$= Z_0 \frac{(Z_L + Z_0) e^{\gamma d} + (Z_L - Z_0) e^{-\gamma d}}{(Z_L + Z_0) e^{\gamma d} - (Z_L - Z_0) e^{-\gamma d}}$$

$$= Z_0 \frac{Z_L (e^{\gamma d} + e^{-\gamma d}) + Z_0 (e^{\gamma d} - e^{-\gamma d})}{Z_L (e^{\gamma d} - e^{-\gamma d}) + Z_0 (e^{\gamma d} + e^{-\gamma d})}$$

$$\left( \text{Use } \cosh(x) \triangleq \frac{e^x + e^{-x}}{2} \quad \text{and} \quad \sinh(x) \triangleq \frac{e^x - e^{-x}}{2} \right)$$

(TL-18)

$$Z(d) = Z_0 \frac{Z_L \cosh(\gamma d) + Z_0 \sinh(\gamma d)}{Z_L \sinh(\gamma d) + Z_0 \cosh(\gamma d)}$$

(divide both num. and denom. by  $\cosh(\gamma d)$ )


$$Z(d) = Z_0 \frac{Z_L + Z_0 \tanh(\gamma d)}{Z_0 + Z_L \tanh(\gamma d)}$$

for a lossy  
( $\alpha \neq 0$ ) T.L.

for a lossless ( $\alpha=0$ ) TL,  $\underline{\alpha=0} \Rightarrow \gamma = j\beta$

$$\Rightarrow \tanh(\gamma d) = \tanh(j\beta d) = j \tan(\beta d)$$
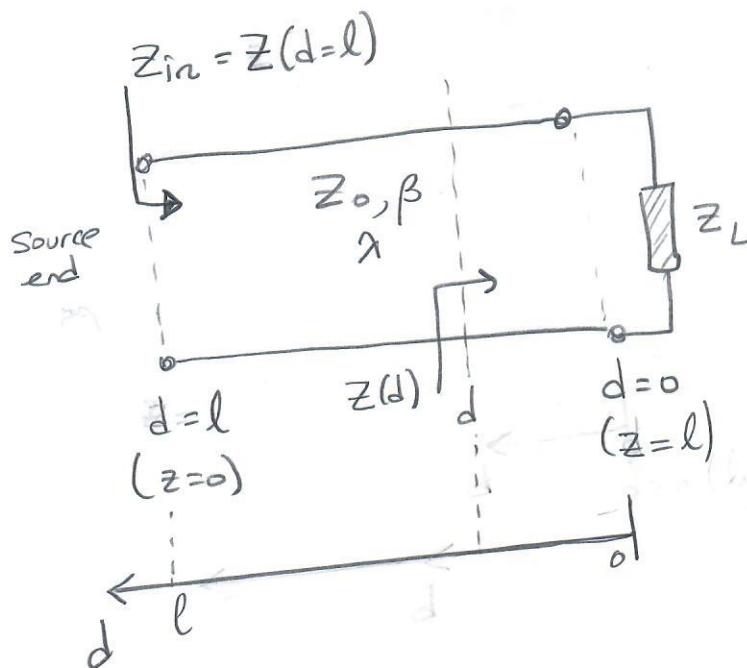
$$\Rightarrow \underset{\text{lossless}}{Z(d)} = Z_0 \frac{Z_L + j Z_0 \tan(\beta d)}{Z_0 + j Z_L \tan(\beta d)}$$



$Z_0$  = characteristic impedance of the T.L.

$\beta$  = Phase constant of the T.L.

$$\beta = \text{Im}\{\gamma\}$$

$$\left( \lambda = \frac{2\pi}{\beta}, v_p = \frac{\omega}{\beta} \right)$$

over the T.L.

## IMPORTANT SPECIAL CASES

### ① Matched Load Case

$$\boxed{Z_L = Z_0}$$

$$\Gamma_L = \frac{Z_L - Z_0}{Z_L + Z_0}$$

$$Z_L = Z_0$$

$$= 0$$

$$\Rightarrow \boxed{\Gamma_L = 0}$$

$$\Gamma(d) = 0$$


$$Z(d) = Z_0$$

for all  $d$

(Remember,  $\Gamma(d) = \Gamma_L e^{-\gamma d} \Big|_{\Gamma_L=0} = 0$  for all  $d$ )

and  $Z(d) = Z_0 \frac{Z_L + Z_0 \tanh(\gamma d)}{Z_0 + Z_L \tanh(\gamma d)} \Big|_{Z_L=Z_0} = Z_0$  for all  $d$ )

Matched  
Line

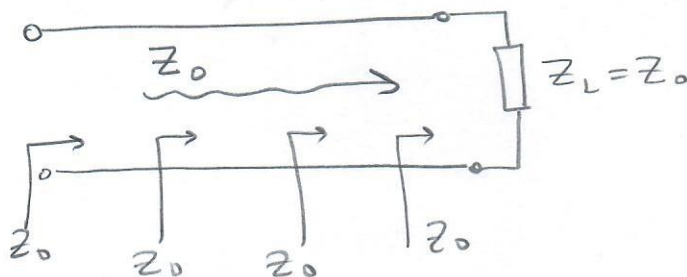

(There is only the  
forward traveling  
wave along the TL)

No reflected wave

### ② Impedance Repeater

$$\text{let } d = \frac{\lambda}{2} \Rightarrow \beta d = \frac{2\pi}{\lambda} d \Big|_{d=\frac{\lambda}{2}} = \frac{2\pi}{\lambda} \frac{\lambda}{2} = \pi$$

$$\beta d = \pi \Rightarrow \tan(\beta d) = \tan(\pi) = 0$$

$$\Rightarrow Z(d = \frac{\lambda}{2}) = Z_0 \frac{Z_L + Z_0 \tan(\beta d)}{Z_0 + Z_L \tan(\beta d)} = Z_L$$

lossless

$$\Rightarrow \boxed{Z_{\text{lossless}} \left(d = \frac{\lambda}{2}\right) = Z_L}$$

In fact, the impedance of a lossless T.L. becomes equal to its load impedance  $Z_L$  periodically at distances  $d = n \frac{\lambda}{2}$  ( $n=1, 2, 3, \dots$ ).

$\Rightarrow$  A lossless T.L. which is  $(n \frac{\lambda}{2})$  long is called an Impedance Repeater as its input impedance  $Z_{\text{in}}(l = n \frac{\lambda}{2})$  is equal to its load impedance  $Z_L$ .

### ③ Impedance Inverter

$$\text{Let } d = \frac{\lambda}{4} \Rightarrow \beta d = \frac{2\pi}{\lambda} \frac{\lambda}{4} = \frac{\pi}{2}$$

$$\Rightarrow \tan(\beta d) = \tan\left(\frac{\pi}{2}\right) \rightarrow \infty$$


$$\Rightarrow Z_{\text{lossless}} \left(d = \frac{\lambda}{4}\right) = \lim_{\tan(\beta d) \rightarrow \infty} Z_0 \frac{Z_L + Z_0 \tan(\beta d)}{Z_0 + Z_L \tan(\beta d)} = \frac{Z_0^2}{Z_L}$$

$$\boxed{Z_{\text{lossless}} \left(d = \frac{\lambda}{4}\right) = \frac{Z_0^2}{Z_L}}$$

A lossless T.L. which is  $(2n+1) \frac{\lambda}{4}$  ( $n=0, 1, 2, \dots$ ) long is called Impedance Inverter as its input impedance is inversely proportional to its load impedance  $Z_L$ .




## Example: Quarter-Wave Transformer

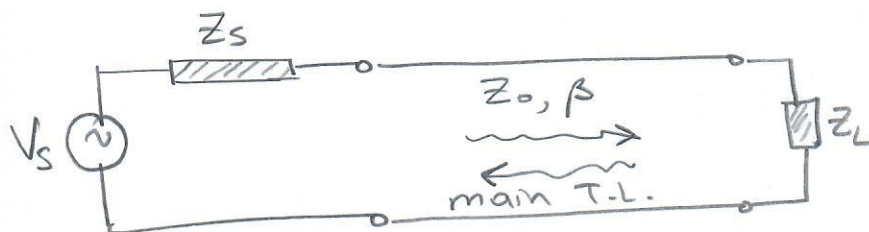

As long as  $Z_L \neq Z_0$ , there will be reflections from the load. These reflections should be minimized to deliver maximum possible power to the load.

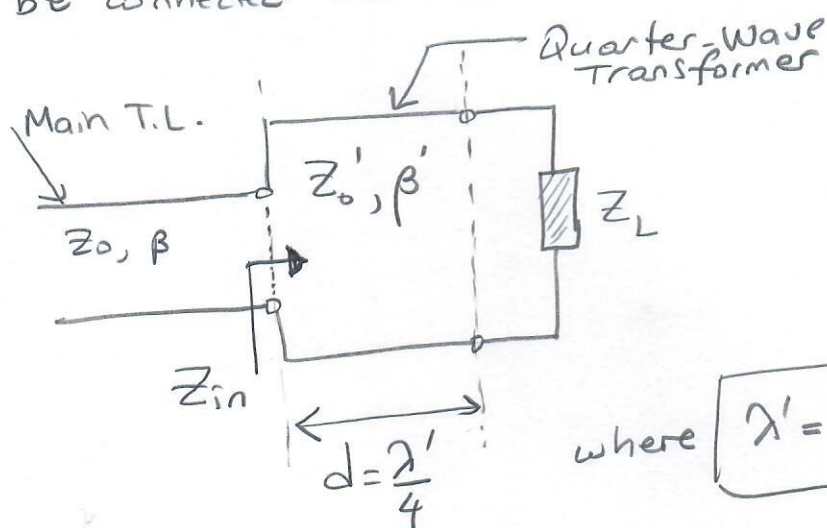As a solution, a quarter-wave length TL can be connected between the "main T.L." and the load  $Z_L$ .



where  $\lambda' = \frac{2\pi}{\beta'}$  ( $\lambda \neq \lambda'_{in}$  general)


To eliminate reflected waves on the main T.L., we must provide  $Z_{in} = Z_0$

where  $Z_{in} = Z(d = \frac{\lambda'}{4}) = \frac{(Z'_0)^2}{Z_L}$   $\left\{ \begin{array}{l} \frac{(Z'_0)^2}{Z_L} = Z_0 \\ \text{is required} \end{array} \right.$

$\Rightarrow$  Choosing  $\begin{cases} d = \lambda'/4 \\ Z'_0 = \sqrt{Z_0 Z_L} \end{cases}$  eliminates reflections on the main line

#### ④ Short-Circuited TL

Let  $Z_L = 0$  (short circuit)

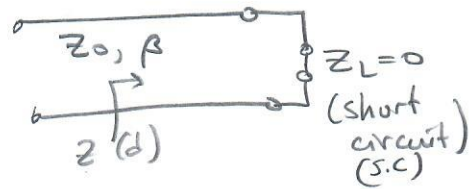

$$\Rightarrow \Gamma_L = \frac{Z_L - Z_0}{Z_L + Z_0} \bigg|_{Z_L=0} = -1 \Rightarrow \boxed{\Gamma_L = -1}$$


$$\Rightarrow Z(d) \bigg|_{Z_L=0} = Z_0 \frac{Z_L + Z_0 \tanh(\gamma d)}{Z_0 + Z_L \tanh(\gamma d)} = Z_0 \tanh(\gamma d)$$

For a lossless T.L.  $\Rightarrow$   
( $\alpha=0$ ,  $\gamma=j\beta$ )

$$\boxed{Z(d)_{\text{lossless}} = j Z_0 \tan(\beta d) = Z_{\text{s.c.}}}$$

#### ⑤ Open-Circuited TL

Let  $Z_L \rightarrow \infty$

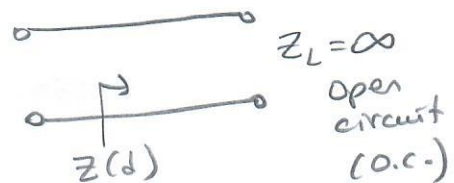

$$\Rightarrow \Gamma_L = \frac{Z_L - Z_0}{Z_L + Z_0} \bigg|_{Z_L \rightarrow \infty} = +1 \Rightarrow \boxed{\Gamma_L = +1}$$

$$\Rightarrow Z(d) \bigg|_{Z_L \rightarrow \infty} = \frac{Z_0}{\tanh(\gamma d)} = Z_0 \coth(\gamma d)$$

For a lossless T.L.  $\Rightarrow$

$$\boxed{Z(d)_{\text{lossless}} = -j Z_0 \cot(\beta d) = Z_{\text{o.c.}}}$$

# Use of short-circuited / open-circuited Transmission Lines to design circuit elements (capacitors/inductors)

As  $f \uparrow \Rightarrow \lambda \downarrow \Rightarrow$  Dimensions of conventional lumped circuit elements like capacitors and inductors become radiating.


$\Rightarrow$  Simple rules of circuit theory can not explain their performance any more.

$\Rightarrow$  As an alternative, short-circuited or open-circuited T.L.s (stubs) can be used as capacitors and inductors at UHF and higher frequencies.

Case I : Consider a lossless T.L. of length  $l < \frac{\lambda}{4}$

for which  $\beta l = \frac{2\pi}{\lambda} l \mid < \frac{\pi}{2}$  (in the first quadrant)  
 $l < \frac{\lambda}{4}$

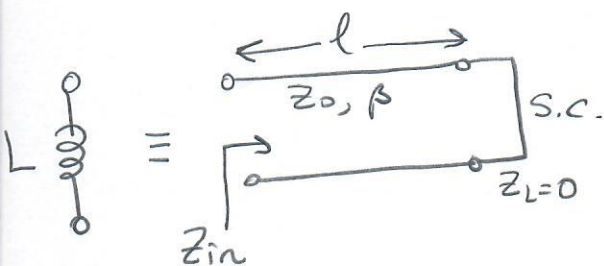
if  $\beta l < \frac{\pi}{2} \Rightarrow \tan(\beta l) > 0$  and  $\cot(\beta l) > 0$



$$Z_{in} = j Z_0 \underbrace{\tan \beta l}_{>0} \equiv j \omega L$$

$$\Rightarrow \boxed{\omega L = Z_0 \tan(\beta l)}$$

using a short-circuited stub!

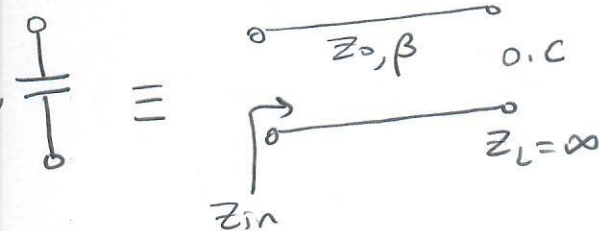




$$Z_{in} = \underbrace{-j Z_0 \cot(\beta l)}_{\text{(minus sign)}} \equiv \frac{1}{j \omega C} = -j \frac{1}{\omega C}$$

$$\Rightarrow \boxed{\frac{1}{\omega C} = Z_0 \cot(\beta l)}$$

using an open-circuited stub




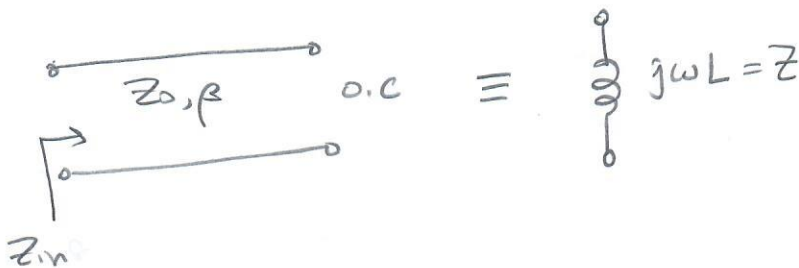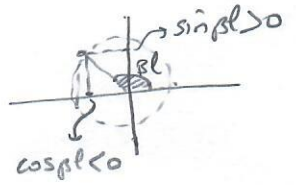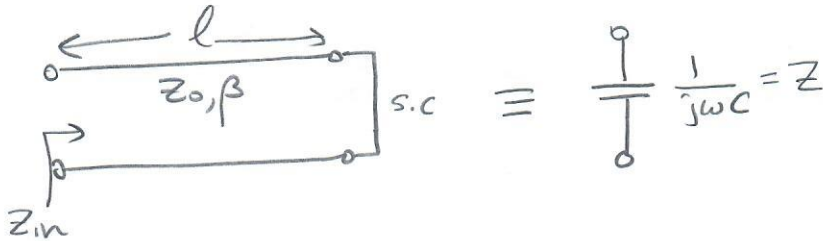Case II : Now consider a lossless T.L. of length  $l$   
 $\beta l = \frac{2\pi}{\lambda} l \Rightarrow \boxed{\frac{\pi}{2} < \beta l < \pi}$  (in the 2nd quadrant)  
 $\frac{\lambda}{4} < l < \frac{\lambda}{2} \Rightarrow \left\{ \begin{array}{l} \tan \beta l < 0 \text{ and } \cot(\beta l) < 0 \end{array} \right.$



Note : Short-circuited stubs with adjustable length " $l$ " are commonly used to produce capacitor/inductor effects.

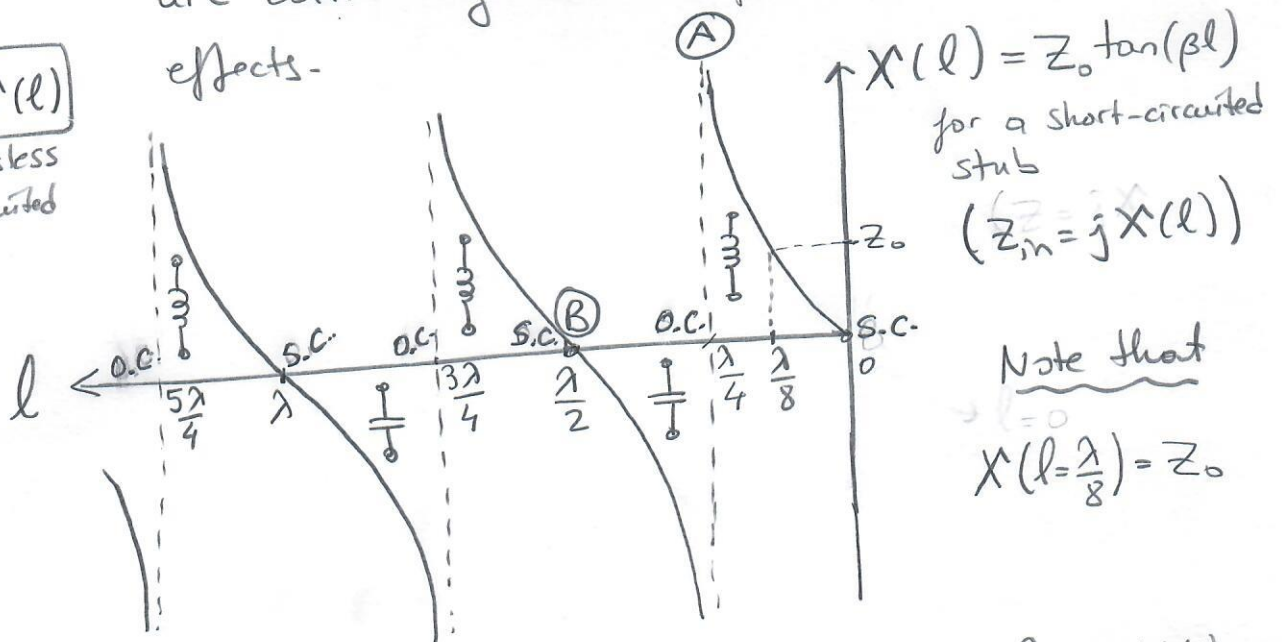
$Z(l) = jX(l)$   
 for a lossless short-circuited T.L.



$X(l) = Z_0 \tan(\beta l)$   
 for a short-circuited stub  
 $(Z_{in} = jX(l))$


Note that  
 $X(l = \frac{\lambda}{8}) = Z_0$

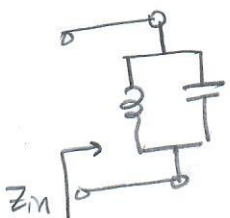at (A)  $l \approx \frac{\lambda}{4} \Rightarrow X(l) \rightarrow \infty$   
 Short-circuited stub behaves like a parallel resonant circuit




at (B)  $l \approx \frac{\lambda}{2} \Rightarrow X(l) \rightarrow 0$

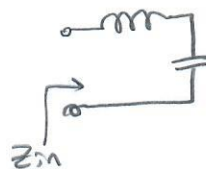Short-circuited stub behaves like a series resonant circuit.





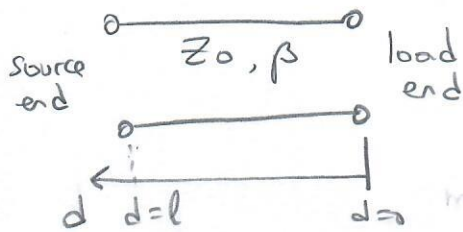Problem: Can we obtain characteristic impedance  $Z_0$  using the short-circuit and open-circuit impedance measurements?



Consider a lossless T.L. Measure (for an arbitrary  $d$ )


$$\begin{aligned} Z_{sc} &= j Z_0 \tan(\beta d) \\ Z_{oc} &= -j Z_0 \cot(\beta d) \end{aligned} \quad \left. \begin{array}{l} \\ \end{array} \right\} \begin{array}{l} \text{multiply} \\ \text{them!} \end{array}$$

$$Z_{sc} Z_{oc} = (j Z_0 \tan \beta d) (-j Z_0 \cot(\beta d)) = Z_0^2$$

$$\Rightarrow \boxed{Z_0 = \sqrt{Z_{sc} Z_{oc}}}$$

Geometric mean of the open circuited impedance and short circuited impedance gives the characteristic imp.

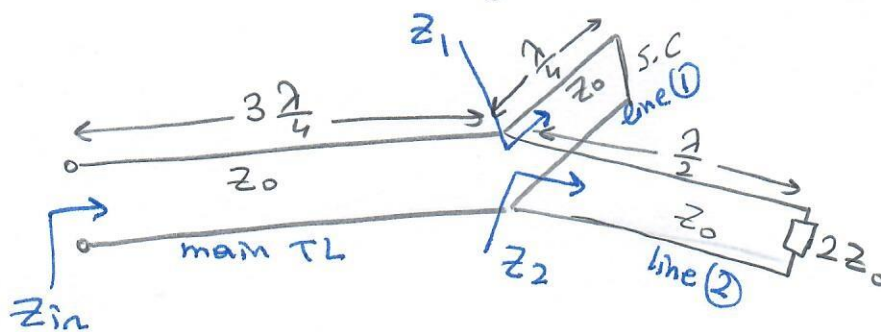Example: Calculate the input impedance  $Z_{in}$  for the following TL configuration.



$Z_1$ : input imp. of TL1

$Z_2$ : input imp. of TL2

$Z'$ : load impedance seen by main TL

TL ①:  $\frac{\lambda}{4}$  long  $\rightarrow$  Impedance inverter, load  $Z_L = 0$  (S.C.)  $\Rightarrow Z_1 = \frac{Z_0^2}{Z_L} = \infty$  (o.c.)

TL ②:  $\frac{\lambda}{2}$  long  $\rightarrow$  Impedance repeater, load  $Z_L = 2Z_0 \Rightarrow Z_2 = Z_L = 2Z_0$

$$Z' = Z_1 \parallel Z_2 = (\infty) \parallel 2Z_0 = 2Z_0 \Rightarrow \boxed{Z' = 2Z_0}$$

TL ① and TL ② are connected in parallel and act like an equivalent load for the main transmission line.

(TL-26)

Main TL:  $\frac{3\lambda}{4}$  long  $\rightarrow$  Impedance Inverter  $\Rightarrow Z_{in} = \frac{Z_0^2}{Z'}$

$$Z_{in} = \frac{Z_0^2}{2Z_0} = \frac{Z_0}{2} \Rightarrow \boxed{Z_{in} = \frac{Z_0}{2}}$$

Note that in this example, we are given three TLs of the same type having the same characteristic impedance  $Z_0$  and the same wavelength  $\lambda$ . In general, however, we could have different  $Z_0$ 's ( $Z_{01}, Z_{02}, Z_{03}$ ) and different  $\beta$  ( $\beta_1, \beta_2, \beta_3$ ) leading to different wavelength values  $\lambda$  ( $\lambda_1, \lambda_2, \lambda_3$ ).

Example: Put an O.C. instead of a S.C. at the end of TL①. Then find  $Z_{in}$  in the problem above.

Answer:  $Z_1 = \left. \frac{Z_0^2}{Z_{L1}} \right|_{Z_{L1} \rightarrow \infty} = 0 \text{ (s.c.)} \Rightarrow Z' = 0 \parallel Z_2 = 0 \text{ (s.c.)}$   
 $\Rightarrow Z_{in} = \left. \frac{Z_0^2}{Z'} \right|_{Z'=0} = \infty \text{ (o.c.)}$

Example ...  $Z_{in}$