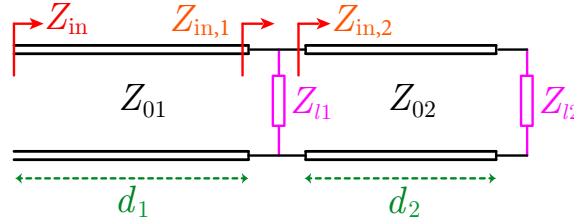


## 2020-2021, EE303 – Recitation 11

### Question 1

Consider a combination of two loads and two lossless transmission lines.



The transmission lines are described as follows:


$$\bullet \quad Z_{01} = 100 \, \Omega, \quad d_1 = \lambda/4, \quad \bullet \quad Z_{02} = 200 \, \Omega, \quad d_2 = 5\lambda/8 \quad (1)$$

Given the load impedances  $Z_{l1} = (100 - j200) \, \Omega$  and  $Z_{l2} = (100 + j100) \, \Omega$ , do the following.

- In the *second* transmission line, find the positions (measured from the load) of the first maximum and the first minimum of the voltage pattern.
- Find VSWR in both transmission lines.
- Find the input impedance of the overall combination, i.e.,  $Z_{in}$ .
- \* Extra question: Is it possible to make VSWR in the first line *unity* by selecting a suitable  $Z_{l1}$  without changing any other item?
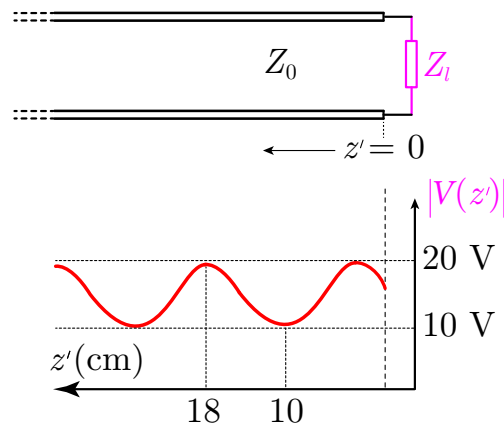
### Question 2

Consider a lossless transmission line terminated by a load  $Z_l$  with a given voltage pattern. Assume that the phase velocity is  $3 \times 10^8$  m/s along the line.



- Find the wavelength and VSWR in the line.
- Find the magnitudes of the incident and reflected voltage waves.
- Find the reflection coefficient at the load ( $\Gamma_l$ ).
- Find the load impedance if the characteristic impedance of the transmission line is  $Z_0 = 200 \Omega$ .
- If the load involves a single inductor or capacitor (in addition to a resistor), find the value of the inductance or capacitance.
- Find the impedance value measured at  $z' = 8 \text{ cm}$ .

### Question 3

A series combination of a  $30 \Omega$  resistor and a  $1/(80\pi)$  nF capacitor is connected to a lossless transmission line as a load at 1 GHz. The characteristic impedance of the transmission line is  $50 \Omega$ , while the phase velocity is  $3 \times 10^8 \text{ m/s}$ . Find the impedance values measured at  $z' = 7.5 \text{ cm}$  and  $z' = 15 \text{ cm}$ . Also find how the values change if the frequency is increased to 2 GHz.