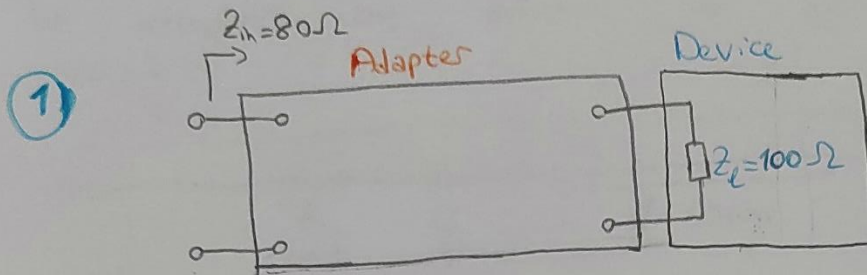


# EE303 HW#9 SOLUTIONS



$f = 1 \text{ GHz}$  and we have

- 50 cm lossless coaxial cable with  $C_c = 25 \text{ pF/m}$  and

$L_c = 62.5 \text{ nH/m}$

-  $40 \text{ } \Omega$  resistor,  $5.3 \text{ pF}$  capacitor and  $12.7 \text{ nH}$  inductor

• For lossless transmission line,

$$Z_0 = \sqrt{\frac{L_c}{C_c}} = \sqrt{\frac{62.5 \times 10^{-9}}{25 \times 10^{-12}}} = 50 \text{ } \Omega$$


$$\beta = \omega \sqrt{L_c C_c} = 2\pi f \sqrt{L_c C_c} = 2\pi \times 10^9 \sqrt{62.5 \times 10^{-9} \times 25 \times 10^{-12}} = 7.854 \text{ rad/m}$$

$$\lambda = \frac{2\pi}{\beta} = \frac{2\pi}{7.854} = 0.8 \text{ m}$$

$$Z_c = \frac{1}{j\omega C} = \frac{1}{j2\pi \times 10^9 \times 5.3 \times 10^{-12}} = -j30 \text{ } \Omega$$

$$Z_L = j\omega L = j2\pi \times 10^9 \times 12.7 \times 10^{-9} = j80 \text{ } \Omega$$

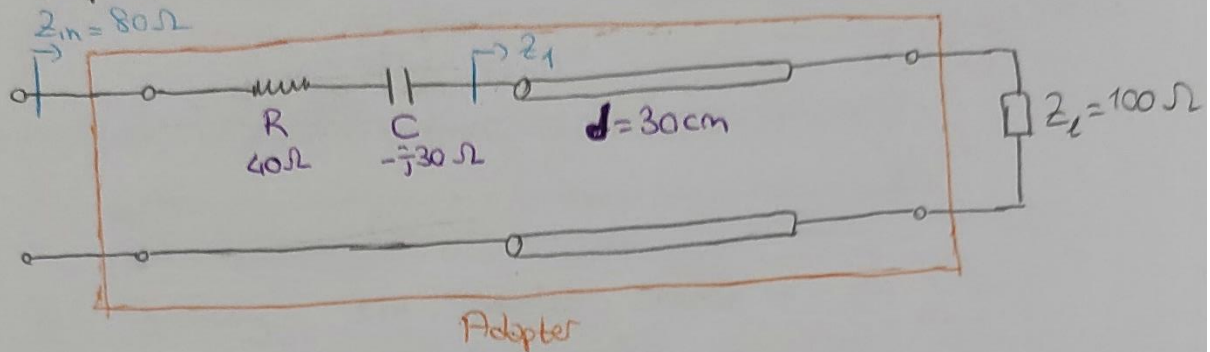- There can be multiple solutions to this design problem and all correct solutions will be acceptable. One solution is given here as an example:



$$Z_1 = Z_0 \left( \frac{Z_L + jZ_0 \tan(\beta d)}{Z_0 + jZ_L \tan(\beta d)} \right)$$

Here,  $Z_0 = 50 \text{ Ohm}$ ,  $Z_L = 100 \text{ Ohm}$ ,  $\beta = 7.854 \text{ rad/m}$


and  $d = 30 \text{ cm} = 0.3 \text{ m}$

$$\text{Then } Z_1 = 50 \left( \frac{100 + j50 \tan(7.854 \times 0.3)}{50 + j100 \tan(7.854 \times 0.3)} \right) = 40 + j30 \text{ } \Omega$$

$$\text{Since } Z_{in} = R + Z_C + Z_1 = 40 + (-j30) + (40 + j30) = 80 \text{ Ohm}$$


the design is successful.

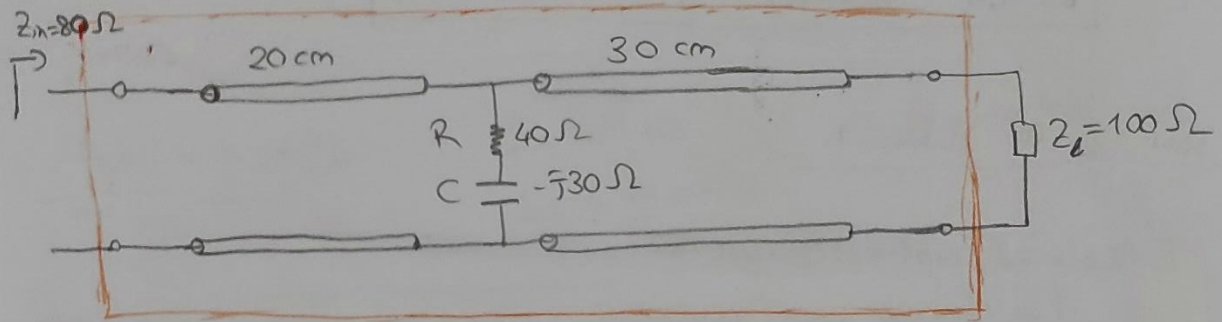an alternative design could be the one shown below:



Adapter

By following the similar procedure, we can confirm that  $Z_{in} = 80 \Omega$  when we use this design.

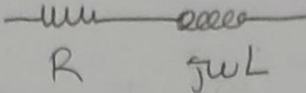② Load : 

$$R = 10 \text{ Ohm}$$

$$j\omega L = j2\pi fL$$

$$f = 10^9 \text{ Hz}$$

$$L = 4.77 \times 10^{-9} \text{ H}$$

$$\Rightarrow j\omega L = j30 \text{ } \Omega$$

$$\boxed{Z_L = R + j\omega L = 10 + j30 \text{ Ohm}} \quad (\text{Load impedance})$$

$Z_0$  is given as  $20 \text{ Ohm}$

$$\bullet \Gamma_L = \frac{Z_L - Z_0}{Z_L + Z_0} = \frac{10 + j30 - 20}{10 + j30 + 20} = \frac{-10 + j30}{30 + j30} = 0.333 + j0.666$$

$$VSWR = \frac{1 + |\Gamma_L|}{1 - |\Gamma_L|} = \frac{1 + |0.333 + j0.666|}{1 - |0.333 + j0.666|} = \boxed{6.85}$$

- $V(z) = V^+ e^{-\gamma z} + V^- e^{\gamma z}$

$\gamma = j\beta$  (for lossless transmission line)

$$\Rightarrow V(z) = V^+ e^{-j\beta z} + V^- e^{j\beta z}$$

When the distance is measured from the load:

$$V(z') = V(z) \Big|_{z=l-z'} = V^+ e^{-j\beta l} e^{j\beta z'} + V^- e^{j\beta l} e^{-j\beta z'}$$

$z'$ : the distance from the load,  $l$ : the length of transmission line

$$V(z') = V^+ e^{-j\beta l} e^{j\beta z'} + V^- e^{j\beta l} e^{-j\beta z'} = V_L^+ e^{j\beta z'} + V_L^- e^{-j\beta z'}$$

( $V_L^+ = V^+ e^{-j\beta l}$  and  $V_L^- = V^- e^{j\beta l}$ )

$$V_L^+ = 1V \quad (\text{given in the question})$$

$$\Gamma_L = \frac{V_L^-}{V_L^+} \Rightarrow V_L^- = V_L^+ \Gamma_L = (0.333 + j0.666) \text{ Volt}$$

$$\Rightarrow V(z') = e^{j\beta z'} \left( 1 + (0.333 + j0.666) e^{-j2\beta z'} \right) \text{ Volt}$$



$$\bullet |V(z')| = \underbrace{|e^{j\beta z'}|}_1 |1 + \Gamma_L e^{-j2\beta z'}| V$$

$\Rightarrow |V(z')|$  becomes maximum when  $|1 + \Gamma_L e^{-j2\beta z'}|$  is maximum.

$$|1 + (0.333 + j0.666) e^{-j2\beta z'}| \text{ is max. for } e^{-j2\beta z'} = \frac{\Gamma_L^*}{|\Gamma_L|}$$

$$\Rightarrow e^{-j2\beta z'_{\max}} = \frac{0.333 - j0.666}{|0.333 + j0.666|}$$

$$\Rightarrow 2\beta z'_{\max} = 1.071 \text{ radian}$$

$\Rightarrow$

$$z'_{\max} = \frac{1.071}{4\pi} \lambda = 0.0852\lambda$$

We know that transmission lines are periodic with  $\frac{\lambda}{2}$ , the set of points, where  $|V(z')|$  is maximum, are  $z' = 0.0852\lambda, 0.5852\lambda, 1.0852\lambda, \dots$

$\begin{matrix} \text{1st} & & \text{2nd} & & \text{3rd} \\ \downarrow & & \downarrow & & \downarrow \\ \text{maximum point} & & & & \end{matrix}$

$|V(z')|$  is minimum when  $|1 + (0.333 + j0.666)e^{-j2\beta z'}|$  is minimum

$$|1 + (0.333 + j0.666)e^{-j2\beta z'}| \text{ is min. for } e^{-j2\beta z'} = \frac{-\Gamma_L}{|\Gamma_L|}$$

$$\Rightarrow e^{-j2\beta z'_{\min}} = \frac{-(0.333 - j0.666)}{|0.333 + j0.666|}$$

$$\Rightarrow 2\beta z'_{\min} = 4.2487 \text{ radian}$$


$$\Rightarrow z'_{\min} = \frac{4.2487}{4\pi} \lambda = 0.3381 \lambda$$

Again, due to periodicity with  $\frac{\lambda}{2}$ , the set of point where  $|V(z')|$  is minimum:

$$z'_{\min} = \underbrace{0.3381\lambda}_{1^{\text{st}} \text{ minimum point}}, 0.8381\lambda, 1.3381\lambda, \dots$$

$$z'_{\min, \text{first}} = 0.3381\lambda, \quad z'_{\max, \text{first}} = 0.0852\lambda$$
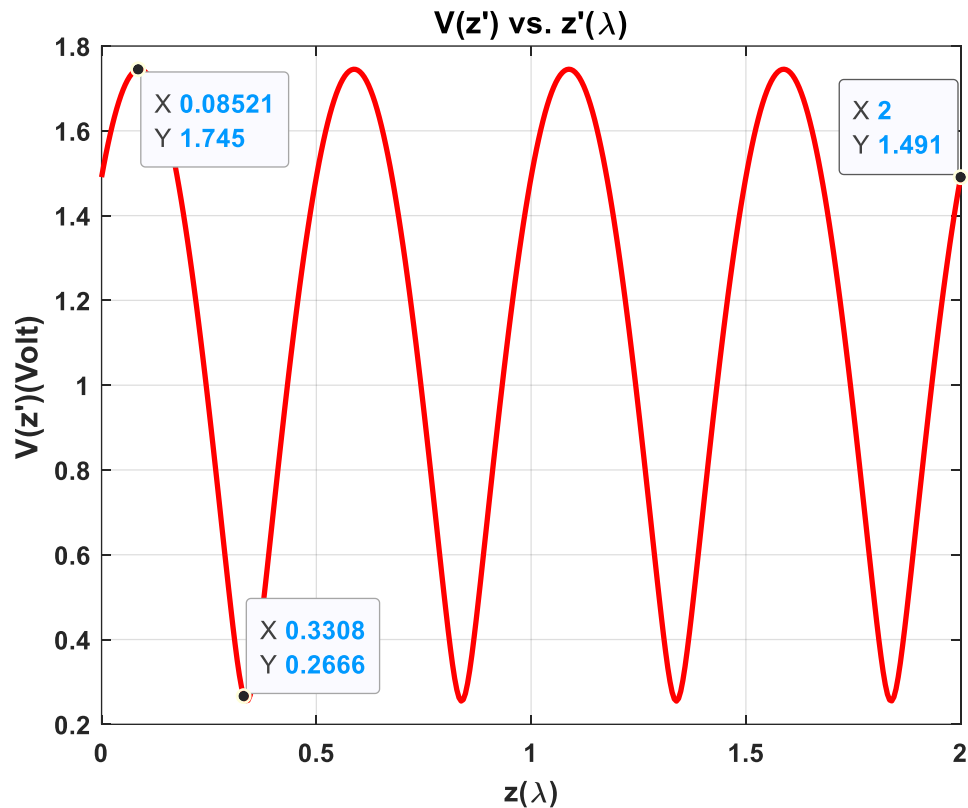
$$z'_{\min, \text{first}} - z'_{\max, \text{first}} = 0.25\lambda \quad \text{as expected} \quad \checkmark$$



•  $V(z') = e^{-j\beta z'} (1 + \Gamma_L e^{-j2\beta z'})$  V in phasor domain

$$V(z', t) = \text{Re} \{ e^{j\omega t} V(z') \}$$



$$\Rightarrow V(z', t) = \text{Re} \{ e^{j(\omega t + \beta z')} + \Gamma_L e^{j(\omega t - \beta z')} \}$$

$$\text{Re} \{ e^{j(\omega t + \beta z')} \} = \cos(\omega t + \beta z')$$

$$\text{Re} \{ (0.333 + j0.666) e^{j(\omega t - \beta z')} \} = 0.333 \cos(\omega t - \beta z') - 0.666 \sin(\omega t - \beta z')$$
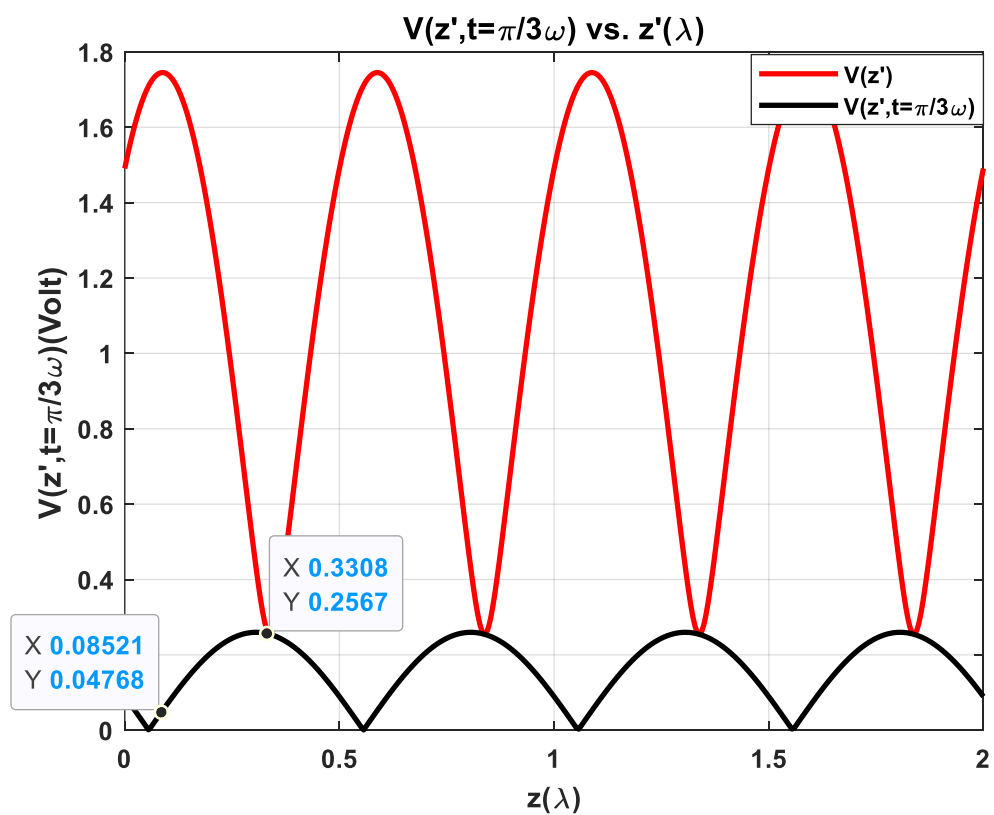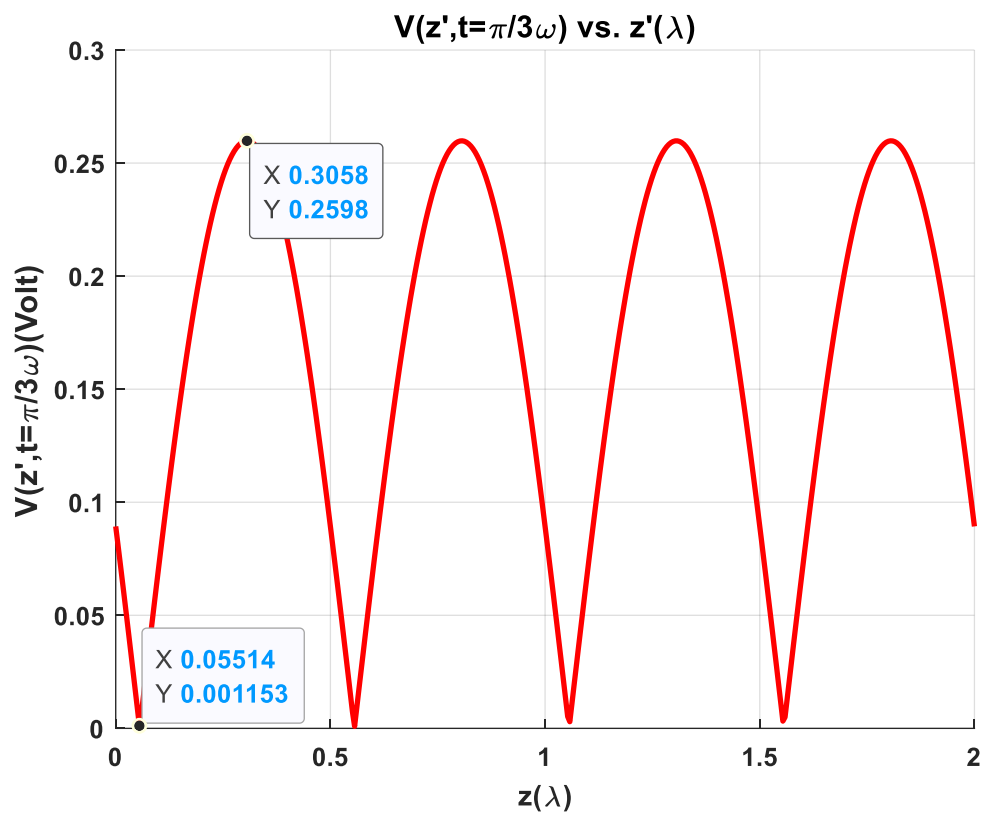
$$\Rightarrow V(z', t) = \cos(\omega t + \beta z') + 0.333 \cos(\omega t - \beta z') - 0.666 \sin(\omega t - \beta z') \quad \text{Volt}$$





By looking at the plot, we can say that

$$|V(z' = z'_{\max, \text{first}}, t = \frac{\pi}{3\omega})| < |V(z' = z'_{\min, \text{first}}, t = \frac{\pi}{3\omega})|$$

$\Rightarrow$  The wave is propagating, not a standing wave,  
so the magnitudes at min & max points change as  
time passes.

MATLAB scripts for plots:

```
clc
clear all
close all

omega=2*pi*1e9; % rad/s
R=10; % Ohm
Z_L=1i*omega*4.77e-9; % Ohm
Z_load=10+30*i; % Ohm
Z0=20; % Ohm
ref_coef_1=(Z_load-Z0)/(Z_load+Z0);

ind_z=1;

% z' is changing from 0 to 2*lambda, so beta*z' is changing from 0 to 4*pi
for beta_z=linspace(0,4*pi,400)

mag_V(ind_z)=abs(1+ref_coef_1*exp(-2i*beta_z)); % magnitude of V(z') Volt

ind_z=ind_z+1;
end

figure
plot(linspace(0,2,400),mag_V,'r','Linewidth',2)
a = get(gca,'XTickLabel');
set(gca,'XTickLabel',a,'FontWeight','bold','FontSize',10);
grid on
xlabel('z (\lambda)')
ylabel('V(z') (Volt)','Fontweight','bold','FontSize',12)
title('V(z') vs. z' (\lambda)','Fontweight','bold','FontSize',12)
```

```

clear all
% close all

omega=2*pi*1e9; % rad/s
R=10; % Ohm
Z_L=1i*omega*4.77e-9; % Ohm
Z_load=10+30*i; % Ohm
Z0=20; % Ohm
ref_coef_l=(Z_load-Z0)/(Z_load+Z0);

ind_z=1;
omega_t=0;

% z' is changing from 0 to 2*lambda, so beta*z' is changing from 0 to 4*pi
for beta_z=linspace(0,4*pi,400)

mag_V(ind_z)=abs((exp(1i*omega_t)*(exp(1i*beta_z)+ref_coef_l*exp(-1i*beta_z)))); % magnitude of V(z') Volt

ind_z=ind_z+1;
end

%hold on
figure
plot(linspace(0,2,400),mag_V,'k','Linewidth',2)
a = get(gca,'XTickLabel');
set(gca,'XTickLabel',a,'FontWeight','bold','FontSize',10);
grid on
xlabel('z(\lambda)')
ylabel('V(z'',t=\pi/3\omega) (Volt)','Fontweight','bold','FontSize',12)
title('V(z'',t=\pi/3\omega) vs. z''(\lambda)','Fontweight','bold','FontSize',12)

% legend('V(z'')','V(z'',t=\pi/3\omega)')

```

③ A rectangular waveguide with  $a = 50 \text{ cm}$   
 $b = 30 \text{ cm}$

$f_{op} = 1.5 \text{ GHz}$  (operating frequency)

First, we need to find cut-off frequencies for possible modes:

Note: TEM wave cannot propagate in rectangular waveguide, so at least one of  $m$  and  $n$  should be greater than 0.

$$f_c = \frac{1}{2\pi\sqrt{\mu\epsilon}} \sqrt{\left(\frac{m\pi}{a}\right)^2 + \left(\frac{n\pi}{b}\right)^2}$$

• For  $m=1, n=0$   $f_c = \frac{1}{2\pi\sqrt{\mu\epsilon}} \sqrt{\left(\frac{\pi}{a}\right)^2} = \frac{1}{2a\sqrt{\mu\epsilon}}$

$\mu = \mu_0$   $\epsilon = \epsilon_0$  for vacuum  $\Rightarrow f_c = 3 \times 10^8 \text{ Hz} < f_{op}$

Thus,  $TE_{10}$  mode can propagate because their cut-off frequencies are below our operating frequency.

• For  $m=0, n=1$   $f_c = \frac{1}{2b\sqrt{\mu\epsilon}} = 5 \times 10^8 \text{ Hz} < f_{op}$

$\Rightarrow TE_{01}$  mode can also propagate.

• For  $m=1, n=1$   $f_c = \frac{1}{2\pi\sqrt{\mu\epsilon}} \sqrt{\left(\frac{\pi}{a}\right)^2 + \left(\frac{\pi}{b}\right)^2} = 5.83 \times 10^8 \text{ Hz} < f_{op}$

$\Rightarrow TE_{11}$  and  $TM_{11}$  can propagate.

\* Remember that for TM waves the fundamental mode is  $TM_{11}$ , so  $m$  and  $n$  cannot be zero for TM.

- For  $m=2, n=0$   $f_c = \frac{1}{2\sqrt{\mu\epsilon}} = 6 \times 10^8 \text{ Hz} < f_{op}$

$\Rightarrow TE_{20}$  can propagate.

- For  $m=0, n=2$   $f_c = \frac{1}{b\sqrt{\mu\epsilon}} = 1 \text{ GHz} < f_{op}$

$\Rightarrow TE_{02}$  can propagate

- For  $m=2, n=1$   $f_c = \frac{1}{2\pi\sqrt{\mu\epsilon}} \sqrt{\left(\frac{2\pi}{a}\right)^2 + \left(\frac{\pi}{b}\right)^2} = 7.81 \times 10^8 \text{ Hz} < f_{op}$

$\Rightarrow TE_{21}$  and  $TM_{21}$  can propagate

- For  $m=1, n=2$   $f_c = \frac{1}{2\pi\sqrt{\mu\epsilon}} \sqrt{\left(\frac{\pi}{a}\right)^2 + \left(\frac{2\pi}{b}\right)^2} = 1.044 \text{ GHz} < f_{op}$

$\Rightarrow TE_{12}$  and  $TM_{12}$  can propagate.

- For  $m=2, n=2$   $f_c = \frac{1}{2\pi\sqrt{\mu\epsilon}} \sqrt{\left(\frac{2\pi}{a}\right)^2 + \left(\frac{2\pi}{b}\right)^2} = 1.166 \text{ GHz} < f_{op}$

$TE_{22}$  and  $TM_{22}$  can propagate

- For  $m=3, n=0$   $f_c = \frac{1}{2\pi\sqrt{\mu\epsilon}} \sqrt{\left(\frac{3\pi}{a}\right)^2} = 9 \text{ GHz} < f_{op}$

$TE_{30}$  can propagate



- For  $m=3, n=1$   $f_c = \frac{1}{2\pi\sqrt{\mu\epsilon}} \sqrt{\left(\frac{3\pi}{a}\right)^2 + \left(\frac{\pi}{b}\right)^2} = 1.029 \text{ GHz}$   
 $f_c < f_{op} \Rightarrow TE_{31}$  and  $TM_{31}$  can propagate
- For  $m=3, n=2$   $f_c = \frac{1}{2\pi\sqrt{\mu\epsilon}} \sqrt{\left(\frac{3\pi}{a}\right)^2 + \left(\frac{2\pi}{b}\right)^2} = 1.345 \text{ GHz} < f_{op}$   
 $\Rightarrow TE_{32}$  and  $TM_{32}$  can propagate
- For  $m=0, n=3$ ,  $f_c = \frac{1}{2\pi\sqrt{\mu\epsilon}} \sqrt{\left(\frac{3\pi}{b}\right)^2} = 1.5 \text{ GHz}$   
 so  $TE_{03}$  cannot propagate.

- For  $m=4, n=0$ ,  $f_c = \frac{1}{2\pi\sqrt{\mu\epsilon}} \sqrt{\left(\frac{4\pi}{a}\right)^2} = 1.2 \text{ GHz} < f_{op}$   
 $TE_{40}$  mode can propagate.
- For  $m=4, n=1$ ,  $f_c = \frac{1}{2\pi\sqrt{\mu\epsilon}} \sqrt{\left(\frac{4\pi}{a}\right)^2 + \left(\frac{\pi}{b}\right)^2} = 1.3 \text{ GHz} < f_{op}$   
 $\Rightarrow TE_{41}$  and  $TM_{41}$  can propagate.
- For  $m=4, n=2$   $f_c = \frac{1}{2\pi\sqrt{\mu\epsilon}} \sqrt{\left(\frac{4\pi}{a}\right)^2 + \left(\frac{2\pi}{b}\right)^2} = 1.562 \text{ GHz}$   
 $\Rightarrow TE_{42}$  and  $TM_{42}$  cannot propagate.

Propagating modes:  $TE_{01}, TE_{10}, TE_{11}, TM_{11}, TE_{02}, TE_{20}, TE_{12},$   
 $TE_{21}, TM_{12}, TM_{21}, TE_{22}, TM_{22}, TE_{03},$   
 $TE_{31}, TM_{31}, TE_{32}, TM_{32}, TE_{40}, TE_{41}, TM_{41}$

Phase constant  $\beta_{mn} = \sqrt{\omega^2 \mu \epsilon - \left(\frac{m\pi}{a}\right)^2 - \left(\frac{n\pi}{b}\right)^2}$

wavelength  $\lambda_{mn} = \frac{2\pi}{\beta_{mn}}$

phase velocity  $v_{mn} = \frac{\omega}{\beta_{mn}}$

MATLAB script to find the modes, phase constants, wavelengths, and phase velocities:

```
clc
clear all

f=1.5e9; % Hz
omega=2*pi*f; % rad/s
a=0.5; % m
b=0.3; % m
for m=0:1:5
    for n=0:1:5

f_c=3e8*(sqrt(((m*pi/a)^2)+((n*pi/b)^2)))/(2*pi); % Hz cut-off frequency
if f>f_c

disp(['when m is ',num2str(m),' and n is ',num2str(n)]);

beta=sqrt((omega^2)/((3e8)^2)-((m*pi/a)^2)-((n*pi/b)^2));
lambda=2*pi/beta;
v=omega/beta;
disp(['phase constant is ',num2str(beta),' rad/m', ' wavelength is ',num2str(lambda),' m', ' and phase velocity is ',num2str(v),' m/s'])
end
end
end
```

Mode	$m, n$	$\beta_{mn}$ (rad/m)	$\lambda_{mn}$ (m)	$v_{mn}$ (m/s)
$TE_{10}$	$m=1$ $n=0$	30.78	0.2041	$3.06 \times 10^8$
$TE_{01}$	$m=0$ $n=1$	29.62	0.2121	$3.18 \times 10^8$
$TE_{11}$ $TM_{11}$	$m=1$ $n=1$	28.95	0.2171	$3.26 \times 10^8$
$TE_{20}$	$m=2$ $n=0$	28.79	0.2182	$3.27 \times 10^8$
$TE_{02}$	$m=0$ $n=2$	23.42	0.2683	$4.025 \times 10^8$
$TE_{21}$ $TM_{21}$	$m=2$ $n=1$	26.82	0.2343	$3.51 \times 10^8$
$TE_{12}$ $TM_{12}$	$m=1$ $n=2$	22.56	0.2785	$4.18 \times 10^8$
$TE_{22}$ $TM_{22}$	$m=2$ $n=2$	19.76	0.3180	$4.77 \times 10^8$
$TE_{30}$	$m=3$ $n=0$	25.13	0.2500	$3.75 \times 10^8$
$TE_{31}$ $TM_{31}$	$m=3$ $n=1$	22.85	0.2750	$4.13 \times 10^8$
$TE_{32}$ $TM_{32}$	$m=3$ $n=2$	13.89	0.4523	$6.78 \times 10^8$
$TE_{40}$	$m=4$ $n=0$	18.85	0.333	$5 \times 10^8$
$TE_{41}$ $TM_{41}$	$m=4$ $n=1$	15.67	0.401	$6.01 \times 10^8$

Throughout the solution I took  $\frac{1}{\sqrt{\mu_0 \epsilon_0}} = 3 \times 10^8 \text{ m/s}$   
but if you take it as  $2.99792 \times 10^8 \text{ m/s}$   
 $\text{TE}_{03}$  mode can propagate, too.