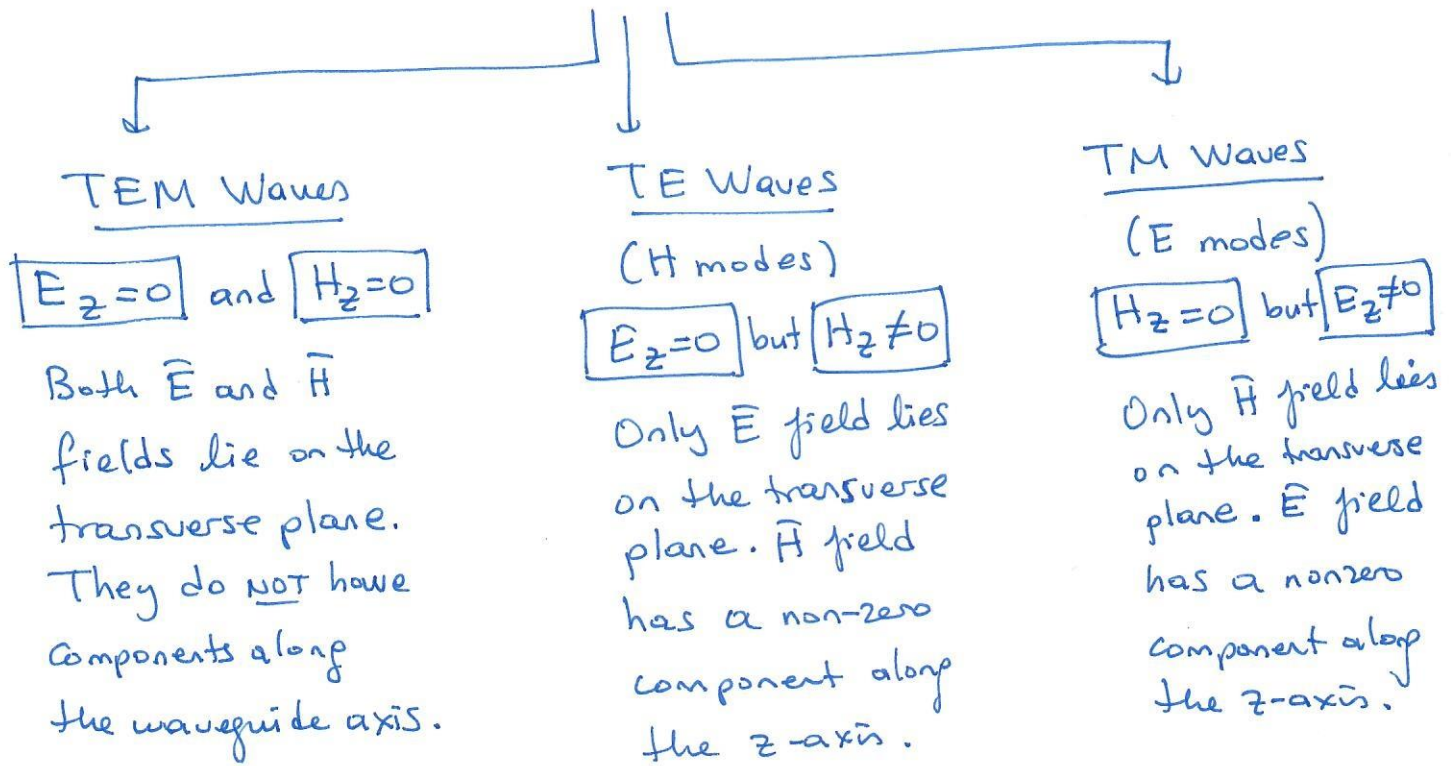


# Classification of Electromagnetic Waves Supported by Waveguiding Structures (extending along the z-axis)



Note: The principal mode in "two-conductor" transmission lines is the TEM mode. When the distance ( $d$ ) between the conductors become larger than  $\frac{\lambda}{4}$ , TE and TM modes become also possible. Such "higher modes" are not desirable in transmission lines, so  $d < \frac{\lambda}{4}$  condition is almost always satisfied.

Note: On the other hand, the waveguides are "single conductor" structures - for that reason, they can NOT carry TEM waves. Only TE and TM modes (waves) can propagate along a waveguide.



## TRANSMISSION LINES

- A transmission line (TL) is a "waveguiding" structure composed of two separate conductors.
- A TL can support the propagation of TEM, TM and TE waves in general. The TEM (Transverse Electromagnetic) mode is the "Principal Mode" of a TL, supported when the distance ( $d$ ) between its conductors is less than  $\frac{\lambda}{4}$ .
- For  $d > \frac{\lambda}{4}$ , TE (Transverse Electric) and TM (Transverse magnetic) modes are also possible but these "higher order" modes are not desired in TL operation.
- While operating with TEM modes,  $\vec{E}$ ,  $\vec{H}$  and  $\hat{n}$  (direction of propagation along the TL) vectors are mutually perpendicular to each other (similar to uniform plane wave propagation).
- Transmission Lines can be analyzed, in general, by using the Electromagnetic Field Theory to determine  $\vec{E}(\vec{r}, t)$  and  $\vec{H}(\vec{r}, t)$ . Alternatively, for the TEM mode operation, transmission lines can be analyzed by using the "circuit theory approach" to determine traveling voltage  $v(z, t)$  and current  $i(z, t)$  waves.
- Let " $l$ " be the length of a given TL. For  $l \ll \frac{\lambda}{4}$  conventional circuit theory can be used. Otherwise, the transmission line theory in terms of traveling voltage and current waves must be used.




# Types of Transmission Lines

## Parallel-plate TLs

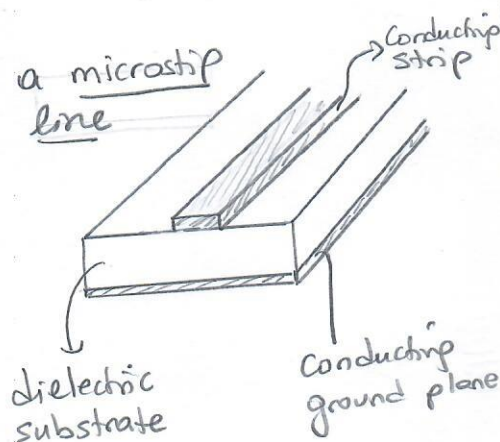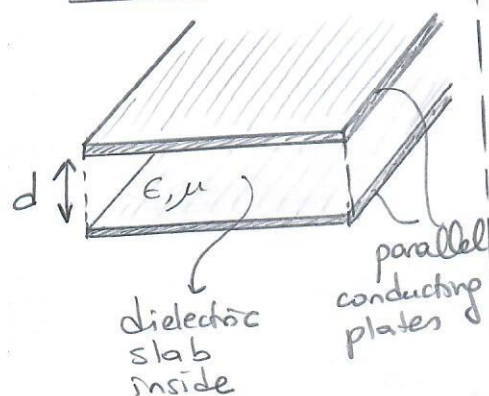


(Strip lines and microstrip lines are types of parallel plate TLs. They can be used at higher microwave frequencies)

## Two-wire TLs

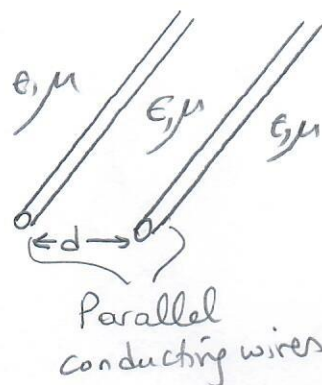

(used in overhead power lines, for ex.)

## Coaxial TLs

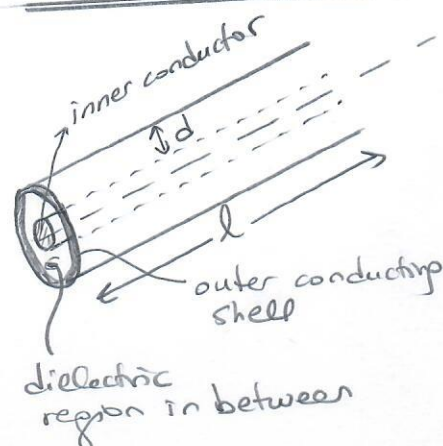

(used in connections between electronic devices such as between the antenna and TV receiver etc.)

- EM fields are confined in the dielectric region
- very small EM Interference from external world.

⊗ If the conductors are not perfect, "conductor losses" occur due to finite conductivity  $\sigma_c < \infty$  of the metal sections. Also, if the dielectric is not perfect, "dielectric losses" occur due to non-zero conductivity  $\sigma_d \neq 0$  of the dielectric section.


Leakage currents exist within lossy dielectrics (i.e. if  $\sigma_d \neq 0$ )

Ex:  
Coaxial TL



$\vec{J} = \sigma_d \vec{E}$  exists if  $\sigma_d \neq 0$   
↓  
cause Joule's heating loss within the dielectric region.
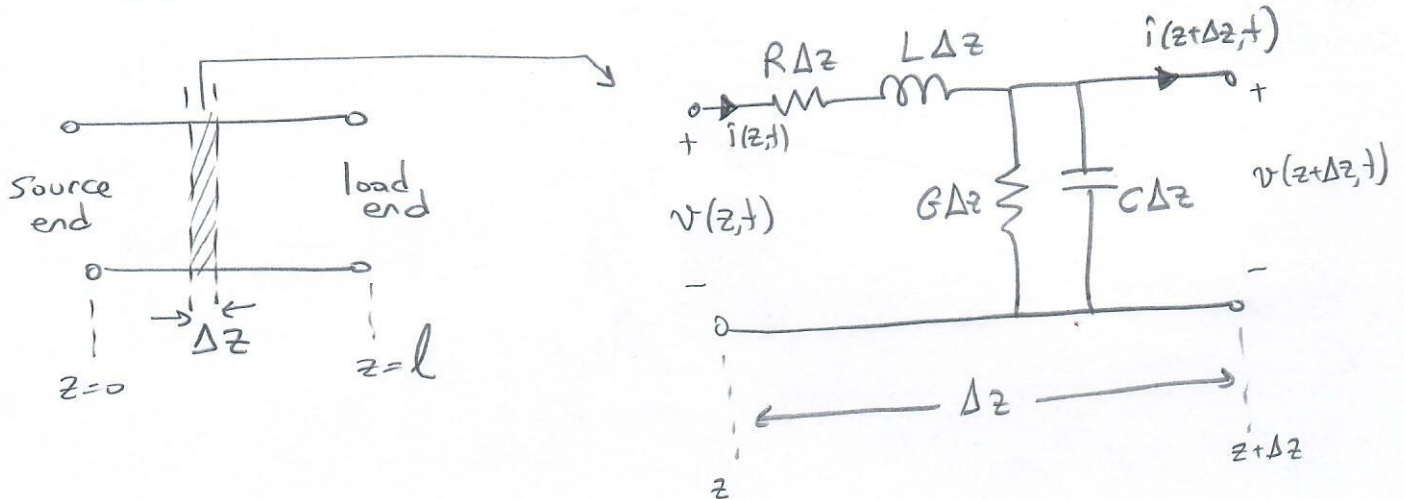
# Use of KVL and KCL to obtain the "Telegrapher's Equation" in Transmission Lines



Distributed parameters of the transmission line

$C$ (F/m)	$L$ (H/m)	$R$ ( $\Omega/m$ )	$G$ (S/m) or ( $S/m$ )
capacitive effects ( $\bar{\epsilon}$ )	inductive effects ( $\bar{\mu}$ )	conductor losses (due to $\sigma_c < \infty$ )	dielectric losses (due to $\sigma_d \neq 0$ )

Apply KVL - Kirchhoff's Voltage Law

$$v(z,t) = (R\Delta z)i(z,t) + (L\Delta z)\frac{\partial i(z,t)}{\partial t} + v(z+\Delta z,t)$$

$$\lim_{\Delta z \rightarrow 0} \left( \frac{v(z,t) - v(z+\Delta z,t)}{\Delta z} \right) = \lim_{\Delta z \rightarrow 0} \left[ \frac{R\Delta z i(z,t) + L\Delta z \frac{\partial i(z,t)}{\partial t}}{\Delta z} \right]$$

$$= -\frac{\partial v(z,t)}{\partial z}$$

$$\Rightarrow \boxed{-\frac{\partial v}{\partial z} = Ri + L \frac{\partial i}{\partial t}} \quad (1)$$

differentiate both sides wrt  $z$   
(also multiply both sides by  $(-1)$ )

$$\boxed{\frac{\partial^2 v}{\partial z^2} = -R \frac{\partial i}{\partial z} - L \frac{\partial^2 i}{\partial z \partial t}} \quad (1')$$



Apply KCL - Kirchoff's Current Law

$$i(z,t) = (G\Delta z)v(z+\Delta z,t) + (C\Delta z)\frac{\partial v(z+\Delta z,t)}{\partial t} + i(z+\Delta z,t)$$

$$\lim_{\Delta z \rightarrow 0} \left[ \frac{i(z,t) - i(z+\Delta z,t)}{\Delta z} \right] = \lim_{\Delta z \rightarrow 0} \left[ \frac{G\Delta z v(z+\Delta z,t) + C\Delta z \frac{\partial v(z+\Delta z,t)}{\partial t}}{\Delta z} \right]$$

$$\underbrace{-\frac{\partial i(z,t)}{\partial z}} = \underbrace{Gv(z,t) + C\frac{\partial v(z,t)}{\partial t}}$$

$$\Rightarrow \boxed{-\frac{\partial i}{\partial z} = Gv + C\frac{\partial v}{\partial t}} \quad (2) \Rightarrow \boxed{-\frac{\partial^2 i}{\partial z \partial t} = G\frac{\partial v}{\partial t} + C\frac{\partial^2 v}{\partial t^2}} \quad (2')$$

differentiate both sides wrt time

Now, substitute  $(-\frac{\partial i}{\partial z})$  from (2) and  $(-\frac{\partial^2 i}{\partial z \partial t})$  from (2') into eqn. (1') to obtain:

$$\frac{\partial^2 v}{\partial z^2} = R(Gv + C\frac{\partial v}{\partial t}) + L(G\frac{\partial v}{\partial t} + C\frac{\partial^2 v}{\partial t^2})$$

Organize this partial differential equation (pde) as


$$\boxed{\frac{\partial^2 v}{\partial z^2} = RGv + (RC + LG)\frac{\partial v}{\partial t} + LC\frac{\partial^2 v}{\partial t^2}}$$

Telegrapher's  
Eqn. for  
 $v(z,t)$   
( $i(z,t)$  satisfies  
the same pde.)

For lossless TLS,  $R=G=0$

$$\Rightarrow \boxed{\frac{\partial^2 v}{\partial z^2} = LC\frac{\partial^2 v}{\partial t^2}} \quad (\text{wave equation for } v(z,t)) \Rightarrow \text{Solution is a traveling wave in the form } f(z \pm vt)$$

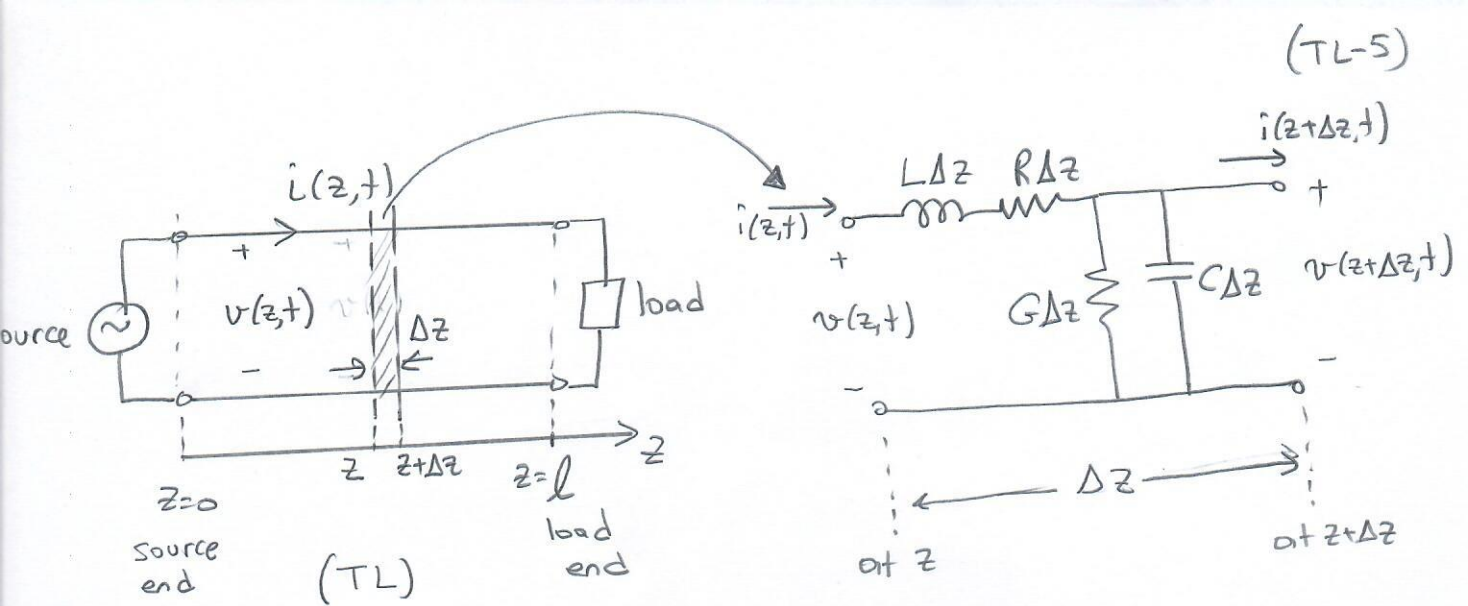with  $v = \frac{1}{\sqrt{LC}}$  velocity.



An infinitesimal section of a T.L. can be represented by a "Distributed Circuit Model" using the "per-unit length" parameters  $R(\Omega/m)$ ,  $L(H/m)$ ,  $C(F/m)$ ,  $G(S/m)$  uniformly and continuously.

Applying the KVL and KCL to the circuit above, it has been shown that we obtain:

$\frac{\partial^2 v}{\partial z^2} = RGv + (RC + LG) \frac{\partial v}{\partial t} + LC \frac{\partial^2 v}{\partial t^2}$	$\left. \begin{array}{l} \text{Telegrapher's} \\ \text{Equations} \\ \text{for} \\ v(z,t) \text{ and } i(z,t) \end{array} \right\}$
$\frac{\partial^2 i}{\partial z^2} = RG i + (RC + LG) \frac{\partial i}{\partial t} + LC \frac{\partial^2 i}{\partial t^2}$	

and

For monochromatic excitation of TLs, phasor domain analysis can be used where  $v(z,t) \leftrightarrow V(z)$  and  $i(z,t) \leftrightarrow I(z)$ .

Therefore, in "AC Steady-State Analysis", letting  $\frac{\partial^n}{\partial t^n} \leftrightarrow (j\omega)^n$

we can get:

$$\frac{d^2 V(z)}{dz^2} = RG V(z) + (RC + LG) j\omega V(z) + LC (j\omega)^2 V(z)$$



$$\frac{d^2 V(z)}{dz^2} - \left[ \underbrace{RG + j\omega RC}_{R(G+j\omega C)} + \underbrace{j\omega LG + (j\omega L)(j\omega C)}_{j\omega L(G+j\omega C)} \right] V(z) = 0$$

$$\boxed{\frac{d^2 V(z)}{dz^2} - [(R+j\omega L)(G+j\omega C)] V(z) = 0}$$

$$\text{let } \boxed{\gamma^2 = (R+j\omega L)(G+j\omega C)} \quad (\gamma: \text{Propagation constant})$$

$$\Rightarrow \boxed{\frac{d^2 V(z)}{dz^2} - \gamma^2 V(z) = 0}$$

needs to be solved  
for the traveling  
voltage phasor  $V(z)$

Then,  $v$

Similarly,

$$\boxed{\frac{d^2 I(z)}{dz^2} - \gamma^2 I(z) = 0}$$

for the traveling  
current phasor  $I(z)$ .

Then  $v(z,t) = \text{Re} \{ V(z) e^{j\omega t} \}$  can be obtained.

and  $i(z,t) = \text{Re} \{ I(z) e^{j\omega t} \}$

$$\frac{d^2 V(z)}{dz^2} - \gamma^2 V(z) = 0 \Rightarrow \boxed{V(z) = V^+ e^{-\gamma z} + V^- e^{\gamma z}}$$

is the general solution  
for  $V(z)$  where  $V^+$  and  $V^-$   
are some arbitrary constants.

$$\text{with } \boxed{\gamma = \sqrt{(R+j\omega L)(G+j\omega C)} = \alpha + j\beta}$$

$\alpha$ : Attenuation constant  
 $\beta$ : Phase constant

Propagation constant  
 $\gamma$  is complex in  
general.

$$V(z) = \underbrace{V^+ e^{-\alpha z} e^{-j\beta z}}_{\substack{\text{forward traveling} \\ \text{wave (in } \hat{a}_z \text{ dir.)} \\ \text{(from source to load)}}} + \underbrace{V^- e^{\alpha z} e^{j\beta z}}_{\substack{\text{backward traveling} \\ \text{wave (in } -\hat{a}_z \text{ dir.)} \\ \text{(from load to source)}}$$

$$v = \frac{\omega}{\text{Im}(\gamma)} = \frac{\omega}{\beta}$$

Velocity of propagation over TL  
(phase velocity)

$$\lambda = \frac{2\pi}{\text{Im}(\gamma)} = \frac{2\pi}{\beta}$$

wavelength of propagation

Compare propagation constants of a TL and a u.p.w

$$\gamma_{TL} = \sqrt{(R + j\omega L)(G + j\omega C)}$$

$$\gamma_{u.p.w} = \sqrt{? j\omega\mu (\sigma + j\omega\epsilon)}$$

No term exists in  $\gamma_{u.p.w}$  corresponding to  $R$  of  $\gamma_{TL}$ ! Why?  
(no conductor losses in u.p.w. propagation in an unbounded lossy space)

Now consider eqn. ① of KVL application:

$$-\frac{\partial v}{\partial z} = Ri + L \frac{\partial i}{\partial t} \longleftrightarrow -\frac{dV(z)}{dz} = RI(z) + j\omega LI(z) = (R + j\omega L)I(z)$$

$$\Rightarrow I(z) = -\frac{1}{R + j\omega L} \frac{dV(z)}{dz}$$

$$= -\frac{1}{R + j\omega L} \frac{d}{dz} [V^+ e^{-\gamma z} + V^- e^{\gamma z}]$$



$$\Rightarrow I(z) = -\frac{1}{R+j\omega L} \left[ -\gamma^1 V^+ e^{-\gamma^1 z} + \gamma^1 V^- e^{\gamma^1 z} \right]$$

$$I(z) = \frac{\gamma^1}{R+j\omega L} \left[ V^+ e^{-\gamma^1 z} - V^- e^{\gamma^1 z} \right]$$

where  $\frac{\gamma^1}{R+j\omega L} = \frac{\sqrt{(R+j\omega L)(G+j\omega C)}}{R+j\omega L} = \sqrt{\frac{G+j\omega C}{R+j\omega L}} \triangleq Y_0$

$$\Rightarrow \boxed{Z_0 \triangleq \frac{1}{Y_0} \triangleq \sqrt{\frac{R+j\omega L}{G+j\omega C}}} \quad \text{Characteristic Impedance of a TL } (\Omega)$$

(Compare with  $\eta_{\text{upw}} = \sqrt{\frac{j\omega\mu}{\sigma+j\omega\epsilon}}$  : intrinsic impedance ( $\Omega$ ) for u.p.w propagation in a lossy medium)

$$\Rightarrow \boxed{I(z) = \frac{1}{Z_0} (V^+ e^{-\gamma^1 z} - V^- e^{\gamma^1 z})}$$

Or define  $\frac{V^+}{Z_0} = I^+$  and  $\frac{-V^-}{Z_0} = I^-$

to write

$$\boxed{I(z) = I^+ e^{-\gamma^1 z} + I^- e^{\gamma^1 z}} \quad \boxed{V(z) = V^+ e^{-\gamma^1 z} + V^- e^{\gamma^1 z}}$$

where  $\frac{V^+}{I^+} = Z_0 = -\frac{V^-}{I^-}$  note the (-) sign!

Note that  $\frac{V(z)}{I(z)} \neq Z_0$  in general

Lossless Transmission Lines  $\leftrightarrow$   $R=0$  and  $G=0$

$$\gamma = \sqrt{(R+j\omega L)(G+j\omega C)} \Big|_{R=G=0} = \sqrt{(j\omega L)(j\omega C)} = j\omega\sqrt{LC} = \gamma_{\text{lossless TL}}$$

$$\gamma = \alpha + j\beta \text{ (in general)} \Rightarrow \begin{cases} \alpha = 0 \\ \beta = \omega\sqrt{LC} \end{cases} \text{ in lossless Transmission Lines!}$$

(Compare to  $\beta_{\text{upw}} = \omega\sqrt{\mu\epsilon}$  in a lossless medium)

$$Z_0 = \sqrt{\frac{R+j\omega L}{G+j\omega C}} \Big|_{R=G=0} = \sqrt{\frac{j\omega L}{j\omega C}} = \sqrt{\frac{L}{C}} \Rightarrow \begin{cases} Z_0 = \sqrt{\frac{L}{C}} \\ \text{lossless TL} \end{cases}$$

(Compare to  $\eta_{\text{upw}} = \sqrt{\frac{\mu}{\epsilon}}$  in a lossless medium)

$$v = \frac{\omega}{\beta} = \frac{\omega}{\omega\sqrt{LC}} = \frac{1}{\sqrt{LC}} \Rightarrow \begin{cases} v_{\text{lossless TL}} = \frac{1}{\sqrt{LC}} \end{cases}$$

(Compare to  $v_{\text{u.p.w}} = \frac{1}{\sqrt{\mu\epsilon}}$  in a lossless medium)

Also,  $\lambda = \frac{2\pi}{\beta} = \frac{2\pi}{\omega\sqrt{LC}} = \frac{2\pi}{2\pi f\sqrt{LC}} = \frac{v}{f}$

$$\text{Also, } \lambda = \frac{2\pi}{\beta} = \frac{2\pi}{\omega\sqrt{LC}} = \frac{2\pi}{2\pi f\sqrt{LC}} = \frac{v}{f} \Rightarrow \boxed{\lambda = \frac{v}{f}}$$

Low-Loss Transmission Lines  $\leftrightarrow$   $\begin{cases} R \ll \omega L \\ G \ll \omega C \end{cases}$

(most TLs behave like this at UHF and above)

$$\gamma = \sqrt{(R+j\omega L)(G+j\omega C)} = \sqrt{\cancel{RG} - \omega^2 LC + j\omega(RC+GL)}$$

negligible w.r.t  $\omega^2 LC$

$$\approx \sqrt{(j\omega)^2 LC + j\omega(RC+GL)} \quad \left( \begin{array}{l} \text{take it to the parenthesis} \\ \text{of } (j\omega)^2 LC = -\omega^2 LC \end{array} \right)$$



$$\gamma \approx j\omega \sqrt{LC} \sqrt{1 - \frac{j\omega(RC + GL)}{\omega^2 LC}}$$

$$= j\omega \sqrt{LC} \sqrt{1 - \underbrace{j\frac{1}{\omega} \left( \frac{R}{L} + \frac{G}{C} \right)}_{\text{very small with respect to 1}}} \quad \left( \begin{array}{l} \text{as } R \ll \omega L \\ \Rightarrow \frac{R}{\omega L} \ll 1 \\ \text{Similarly, } \frac{G}{\omega C} \ll 1 \end{array} \right)$$

Use Binomial Theorem to approximate the square-root term as

$$\sqrt{1-a} \approx 1 - \frac{a}{2} \quad \text{where } \begin{cases} a = \frac{j}{\omega} \left( \frac{R}{L} + \frac{G}{C} \right) \\ \text{and } |a| \ll 1 \end{cases}$$

$$\Rightarrow \gamma \approx j\omega \sqrt{LC} \left[ 1 - \frac{j}{2\omega} \left( \frac{R}{L} + \frac{G}{C} \right) \right] \quad \left( \begin{array}{l} \text{write in the} \\ \gamma = \alpha + j\beta \\ \text{form} \end{array} \right)$$

$$\Rightarrow \gamma \approx \frac{1}{2\omega} \omega \sqrt{LC} \left( \frac{R}{L} + \frac{G}{C} \right) + j\omega \sqrt{LC}$$

$$\gamma \approx \underbrace{\frac{1}{2} \left( R \sqrt{\frac{C}{L}} + G \sqrt{\frac{L}{C}} \right)}_{\alpha} + j \underbrace{\omega \sqrt{LC}}_{\beta} = \alpha + j\beta$$

$$\Rightarrow \boxed{\begin{array}{l} \alpha \approx \frac{1}{2} \left( R \sqrt{\frac{C}{L}} + G \sqrt{\frac{L}{C}} \right) = \frac{1}{2} \left( \frac{R}{Z_0} + G Z_0 \right) \\ \beta \approx \omega \sqrt{LC} \end{array}} \quad \left( \begin{array}{l} \text{for low-loss} \\ \text{transmission} \\ \text{lines.} \\ \text{(where } Z_0 = \sqrt{\frac{L}{C}} \text{)} \\ \downarrow \\ \text{see page} \\ \text{(TL-11)} \end{array} \right)$$

$$\gamma = \alpha + j\beta$$

Note that  $\beta_{\text{lossless TL}} \approx \beta_{\text{low-loss TL}} = \omega \sqrt{LC}$

$\Rightarrow$  expressions for  $v = \frac{\omega}{\beta}$  and  $\lambda = \frac{2\pi}{\beta}$  are also approximately the same in lossless and low-loss transmission line cases!

Also,  $Z_0 = \sqrt{\frac{R+j\omega L}{G+j\omega C}} = \sqrt{\frac{j\omega L (1 + \frac{R}{j\omega L})}{j\omega C (1 + \frac{G}{j\omega C})}}$

$$= \sqrt{\frac{L}{C}} \left(1 + \frac{R}{j\omega L}\right)^{\frac{1}{2}} \left(1 + \frac{G}{j\omega C}\right)^{-\frac{1}{2}}$$

$\underbrace{\frac{R}{j\omega L}}_{\text{very small wrt unity}}$ 
 $\underbrace{\frac{G}{j\omega C}}_{\text{very small wrt unity}}$

(applying Binomial Thm. again)

$$Z_0 \approx \sqrt{\frac{L}{C}} \left(1 + \frac{R}{2j\omega L}\right) \left(1 - \frac{G}{2j\omega C}\right)$$

$$\approx \sqrt{\frac{L}{C}} \left[ 1 + \frac{1}{2j\omega} \left( \frac{R}{L} - \frac{G}{C} \right) + \frac{RG}{4\omega^2 LC} \right]$$

$\underbrace{\frac{1}{2j\omega} \left( \frac{R}{L} - \frac{G}{C} \right)}_{\text{a very small reactive part!}}$ 
 $\frac{RG}{4\omega^2 LC}$   
negligible (very small)

$$Z_0 \approx \sqrt{\frac{L}{C}} - j \frac{1}{2} \sqrt{\frac{L}{C}} \left( \frac{R}{\omega L} - \frac{G}{\omega C} \right)$$

a very small reactive part which is usually neglected

$$Z_0 \approx \sqrt{\frac{L}{C}}$$

as in the lossless TL case.

Exercise Problem = Distortionless Transmission Line

Show that for the condition  $\boxed{\frac{R}{L} = \frac{G}{C}}$ , we'll obtain:

$$\gamma = \sqrt{\frac{C}{L}} (R + j\omega L) = \alpha + j\beta$$

$\alpha = R \sqrt{\frac{C}{L}}$

independent of frequency

$\beta = \omega \sqrt{LC}$

linear function of frequency

$$\Rightarrow v = \frac{\omega}{\beta} = \frac{1}{\sqrt{LC}} \quad (\text{independent of frequency})$$

Also,  $\boxed{Z_0 = \sqrt{\frac{R}{G}} = \sqrt{\frac{L}{C}}}$


as in the lossless case.

• All frequency components of an input wave travel at the same speed ( $v$ ) experiencing the same attenuation ( $\alpha$ )  $\Rightarrow$  NO SIGNAL DISTORTION!



⊛ Study section 8-3 in Cherg for TL parameters!

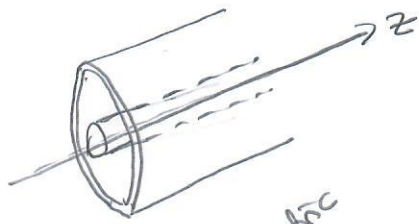
Example: Distributed Parameters of a Coaxial TL



Inner conductor radius =  $a$

Outer conducting shell radius =  $b$

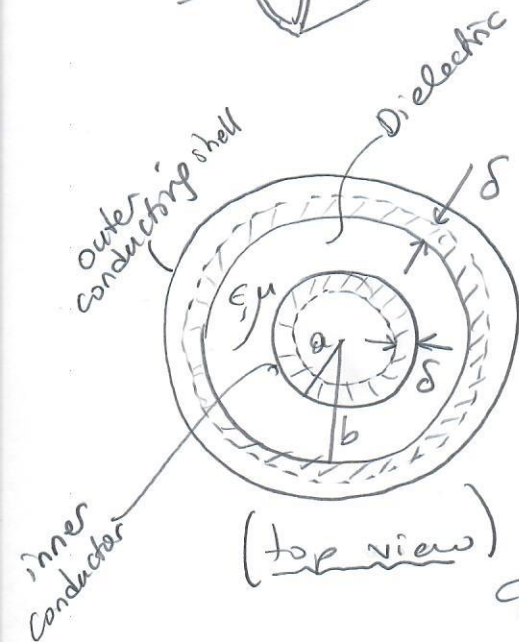Filled by a dielectric ( $\epsilon, \mu$ )



$$L = \frac{\mu}{2\pi} \ln\left(\frac{b}{a}\right) \text{ (H/m)}$$

$$C = \frac{2\pi\epsilon}{\ln\left(\frac{b}{a}\right)} \text{ (F/m)}$$

Characteristic Impedance  $\leftarrow Z_0 = \sqrt{\frac{L}{C}} = \dots = \sqrt{\frac{\mu}{\epsilon}} \frac{\ln(b/a)}{2\pi} \text{ (}\Omega\text{)}$

Phase velocity  $\leftarrow v = \frac{1}{\sqrt{LC}} = \dots = \frac{1}{\sqrt{\mu\epsilon}}$  : velocity of a plane wave in an unbounded medium with parameters  $\epsilon, \mu$ .

$$R = R_{in} + R_{out}$$

$$R = \frac{1}{\sigma_c (2\pi a \delta)} + \frac{1}{\sigma_c (2\pi b \delta)} \text{ (}\Omega/\text{m)}$$

AC resistance of the conductors (per unit length, for  $l=1\text{m}$ )

where  $\delta = \frac{1}{\sqrt{\pi f \mu_c \sigma_c}}$  assuming a well developed skin effect.

$\sigma_c$  = conductance of the conductors,  $\sigma_c < \infty$  but it is very large.

and  $G = \frac{2\pi\sigma_d}{\ln\left(\frac{b}{a}\right)} \text{ (S/m)}$

where  $\sigma_d \neq 0$  but small (conductivity of the dielectric).