

$$\frac{\partial^2 \psi}{\partial z^2} = R G i + (R C + L G) \cdot \frac{di}{dt} + L C \cdot \frac{d^2 i}{dt^2} \quad \left. \right\} \text{Telegrapher's Equations}$$



$$\gamma^2 = (R+jWL)(G+jWC)$$

$$\gamma = \alpha + j\beta$$

$$V(z) = V^+ e^{-\alpha z} e^{j\beta z} + V^- e^{\alpha z} e^{-j\beta z}$$

$$\frac{d^2 V(z)}{dz^2} - \gamma^2 V(z) = 0$$

$$\frac{d^2 I(z)}{dz^2} - \gamma^2 I(z) = 0$$

$$V(z) = V^+ e^{-\gamma z} + V^- e^{\gamma z}$$

$$R = \frac{w}{Im(\gamma)} = \frac{w}{\beta}$$

$$\lambda = \frac{2\pi}{Im(\gamma)} = \frac{2\pi}{\beta}$$

$$Z_0 \triangleq \frac{1}{Y_0} \triangleq \sqrt{\frac{R+jWL}{G+jWC}} \rightarrow \text{char impedance}$$

Lossless

$$\gamma = j\omega \sqrt{LC} \Rightarrow \alpha = 0 \quad Z_0 = \sqrt{\frac{L}{C}} \quad \mu_{upw} = \sqrt{\frac{\mu}{\epsilon}} \quad \beta = \frac{\omega}{\beta} = \frac{\omega}{\sqrt{LC}}$$

$$\text{Also, } \lambda = \frac{2\pi}{\beta} = \frac{2\pi}{\omega \sqrt{LC}} = \frac{2\pi}{2\pi f \sqrt{LC}} = \frac{f}{f} \Rightarrow \lambda = \frac{f}{f}$$

Low loss

$$\gamma = \frac{1}{2} \left(R \underbrace{\sqrt{\frac{C}{L}}} \alpha + G \underbrace{\sqrt{\frac{L}{C}}} \beta \right) + j\omega \sqrt{LC} = \alpha + j\beta$$

$$\alpha = \frac{1}{2} \left(\frac{R}{Z_0} + G \cdot Z_0 \right) \quad \beta = \omega \sqrt{LC} \quad Z_0 \approx \sqrt{\frac{L}{C}}$$

Reflection Coeff

$$V_L = V_L^+ + V_L^-$$

$$\Gamma_L \triangleq \frac{V_L^-}{V_L^+}$$

$$V_S = V(z=0) = V^+ + V^-$$

$$V_L = V(z=L) = \underbrace{V^+ e^{-\gamma L}}_{V_L^+} + \underbrace{V^- e^{+\gamma L}}_{V_L^-} = V_L^+ + V_L^-$$

$$\Gamma_L = \Gamma_L^+ + \Gamma_L^- = \frac{V_L^+}{Z_0} - \frac{V_L^-}{Z_0}$$

$$\frac{V_L}{\Gamma_L} = Z_L$$

$$Z_L = Z_0 \cdot \frac{1 + \Gamma_L}{1 - \Gamma_L} \quad \text{where } \Gamma_L \text{ is complex}$$

$$\Gamma_L = \frac{Z_L - Z_0}{Z_L + Z_0} = |\Gamma_L| \cdot e^{j\theta_L} \iff \Gamma(d) = \Gamma_L \cdot e^{-2\gamma d} \quad \text{where}$$

$$\left. \begin{cases} \gamma = \alpha + j\beta \\ \Gamma_L = |\Gamma_L| \cdot e^{j\theta_L} \end{cases} \right\}$$

$$\Gamma(d) = |\Gamma_L| \cdot e^{-2\alpha d} \cdot e^{j(\theta_L - 2\beta d)}$$

To make complete rotation $2\beta d = 2\pi \quad \frac{2\cdot 2\pi}{\lambda} \cdot d = 2\pi \quad \underline{\underline{d = \frac{\lambda}{2}}}$

$$|\Gamma(d)| = |\Gamma_L| \cdot e^{j2\alpha d} \rightarrow \text{lossy medium}$$

$$\cosh = \frac{e^x + e^{-x}}{2} \quad \sinh = \frac{e^x - e^{-x}}{2}$$

IMPEDANCE

$$Z(d) = Z_0 \cdot \frac{Z_L + jZ_0 \cdot \tan(\beta d)}{Z_0 + jZ_L \cdot \tan(\beta d)}$$

Lossless

lossy
If it is
 $\rightarrow Z(d) = Z_0 \cdot \frac{Z_L + Z_0 \cdot \tanh(\delta d)}{Z_0 + Z_L \cdot \tanh(\delta d)}$

Important Special Cases

1) Matched Load Case $\underline{\underline{Z_L = Z_0}}$

$$\Gamma_L = 0 \Rightarrow \Gamma_L = 0 \rightarrow \text{for all } d \quad Z(d) = Z_0 \quad \rightarrow \text{No reflected wave}$$

2) Impedance Repeater

$$\text{Let } d = \frac{\lambda}{2} \quad \beta d = \frac{2\pi}{\lambda} \cdot d \Big|_{\frac{\lambda}{2}} = \pi = \beta d \quad \tan(\beta d) \Rightarrow 0$$

$$Z_L(d = \frac{\lambda}{2}) = Z_0 \cdot \frac{Z_L + Z_0(0)}{Z_0 + Z_L(0)} = \underline{\underline{Z_L}} \quad d = n \cdot \frac{\lambda}{2} \quad (n = 1, 2, 3, \dots)$$

3) Impedance Inverter

$$\text{Let } d = \frac{\lambda}{4} \quad \beta d = \frac{2\pi}{\lambda} \cdot \frac{\lambda}{4} = \frac{\pi}{2}$$

$$Z_L(d = \frac{\lambda}{4}) = \frac{Z_L + Z_0 \tan \frac{\pi}{2}}{Z_0 + Z_L \tan \frac{\pi}{2}} \cdot Z_0 = \underline{\underline{\frac{Z_0^2}{Z_L}}}$$

A lossless TL which is $(2n+1) \cdot \frac{\lambda}{4}$ ($n = 0, 1, 2, 3, \dots$)

4) Short Circuited TL $\underline{\underline{Z_L = 0}}$ $\Gamma_L = -1$ $Z(d) \Big|_{Z_L=0} = Z_0 \cdot \tanh(\delta d)$

For a lossless TL $\rightarrow Z(d) = j \cdot Z_0 \cdot \tan(\beta d) = Z_{sc}$

5) Open Circuited

$$\text{Let } Z_L \rightarrow \infty \quad \Gamma_L = \frac{Z_L - Z_0}{Z_L + Z_0} \Big|_{Z_L \rightarrow \infty} = 1 \quad \underline{\underline{\Gamma_L = 1}}$$

$$\left. Z(d) \right|_{Z_L \rightarrow \infty} = \frac{Z_0}{\tanh(\beta d)} = Z_0 \coth(\beta d) \quad \xrightarrow{\text{lossless}} Z(d) = -j \cdot Z_0 \cdot \cot(\beta d) = Z_{oc}$$

CASE I

Consider a lossless π_L of $l < \frac{\lambda}{4}$

$$\beta l < \frac{\lambda}{2} \quad \tan(\beta l) > 0 \quad \text{and} \quad \cot(\beta l) > 0$$

$$\text{Short Circuit} \rightarrow Z_{in} = j \cdot Z_0 \cdot \tan(\beta l) = j w L$$

$$\text{Open circuit} \rightarrow Z_{in} = -j \cdot Z_0 \cdot \cot(\beta l) = \frac{1}{j w C} = j \cdot \frac{1}{w C}$$


CASE II

$$\frac{\lambda}{4} < l < \frac{\lambda}{2} \quad \frac{\pi}{2} < \beta l < \pi \quad \tan(\beta l) < 0 \quad \cot(\beta l) < 0$$

Note: Short-circuited stubs with adjustable length "l" are commonly used to produce capacitor/inductor effects.

$$Z(l) = j X(l)$$

for a lossless short-circuited T-L.

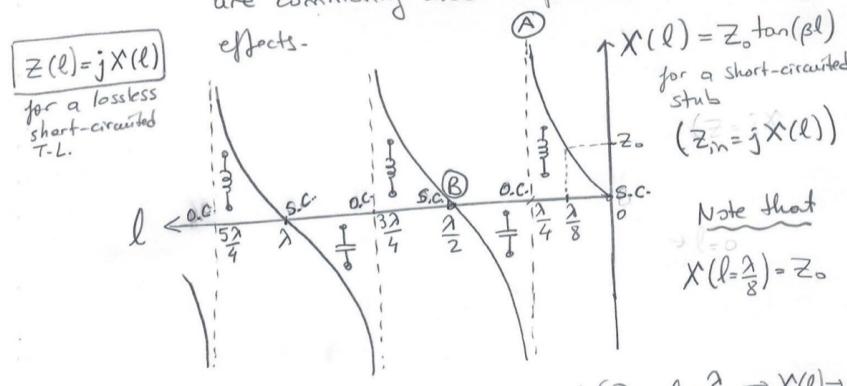

at (A) $l \approx \frac{1}{4} \Rightarrow X(l) \rightarrow \infty$
Short-circuited stub behaves like a parallel resonant circuit

at (B) $l \approx \frac{1}{2} \Rightarrow X(l) \rightarrow 0$
Short-circuited stub behaves like a series resonant circuit.

$$Z_{sc} = j \cdot Z_0 \cdot \tan(\beta l)$$

$$Z_{oc} = -j \cdot Z_0 \cdot \cot(\beta l)$$

$$Z_0 = \sqrt{Z_{sc} \cdot Z_{oc}}$$

STANDING WAVES

Assume π_L is lossless

$$V(d) = V_L^+ \cdot e^{j \beta d} + V_L^- \cdot e^{-j \beta d}$$

$$V(d) = V_L^+ \left(e^{j \beta d} + \frac{V_L^-}{V_L^+} \cdot e^{-j \beta d} \right)$$

$\frac{V_L^-}{V_L^+} \triangleq P_L$

$$Z = l - d$$

$$V(d) = V_+ \cdot e^{-j \beta Z} + V_- \cdot e^{j \beta Z}$$

$$V_L^+ = V^+ \cdot e^{-j \beta l}$$

CASE 1

$$R_L = \frac{Z_L - Z_0}{Z_L + Z_0} \Big|_{Z_L=0} = -1 \Rightarrow R_L = -1$$

$$V(d) = V_L^+ \left(e^{j\beta d} + (-1) \cdot e^{-j\beta d} \right) = 2j \cdot V_L^+ \cdot \sin \beta d$$

$2j \cdot \sin(\beta d)$

$$|V(d)| = 2|V_L^+| \cdot |\sin \beta d| \quad \begin{aligned} &\xrightarrow{\beta d = 0} |V(d)|_{\max} = 2|V_L^+| = V_{\max} \\ &\xrightarrow{\beta d = \pi} |V(d)|_{\min} = 2|V_L^-| = V_{\min} = 0 \end{aligned}$$

DEFINE VSUR

$$S = \frac{V_{\max}}{V_{\min}} \Rightarrow \frac{2V_L^+}{0} = \infty \Rightarrow \text{For short-circuit termination}$$

$S = \infty \quad Z_L = 0$

CASE 2

Open circuit

$$R_L = \frac{Z_L - Z_0}{Z_L + Z_0} = 1 \quad R_L = 1$$

$$V(d) = V_L^+ \left(e^{j\beta d} + (1) \cdot e^{-j\beta d} \right) = 2V_L^+ \cdot \cos \beta d$$

$2 \cdot \cos(\beta d)$

$$|V(d)| = 2|V_L^+| |\cos \beta d| \quad \begin{aligned} &\xrightarrow{\beta d = 0} |V(d)|_{\max} = 2|V_L^+| \\ &\xrightarrow{\beta d = \pi} |V(d)|_{\min} = V_{\min} = 0 \end{aligned}$$

$$S = \infty \quad Z_L = \infty$$

CASE 3 Arbitrary Load Impedance Z_L

$$R_L = \frac{Z_L - Z_0}{Z_L + Z_0} = |R_L| \cdot e^{j\theta_L} \quad |R_L| < 1$$

$$|V_L^+| = |V^+ \cdot e^{j\theta_L}| = |V^+ \cdot e^{j\alpha L} \cdot e^{-j\beta L}| = |V_L^+| \cdot e^{-j\alpha L} \quad \begin{aligned} &\xrightarrow{\text{lossy}} \\ &\downarrow \quad \text{for lossless} \quad \rightarrow |V_L^+| = |V_L^+| \\ &|\cos(\beta L) + j \cdot \sin(\beta L)| = 1 \quad |V_L^-| = |V_L^-| \end{aligned}$$

$$V_{\max} = |V^+| + |V^-| \quad V_{\min} = |V^+| - |V^-| \quad |\Gamma| = \frac{|V^-|}{|V^+|}$$

$$S = \frac{V_{\max}}{V_{\min}} \quad \text{In phase} \quad \text{out of phase}$$

$$|\Gamma(\alpha)| = |\Gamma_L| |e^{-2\alpha d}| \rightarrow \text{lossy TL if } \alpha=0 \rightarrow |\Gamma(\alpha)| = |\Gamma_L|$$

$$\downarrow$$

$$S = \frac{1 + |\Gamma_L|}{1 - |\Gamma_L|}$$

Note that $VSWR \geq 1$ always

$$\frac{1 \leq S < \infty}{\text{Happens for a matched load}}$$

$$\text{happens whenever } |\Gamma_L| = 1$$

$$\left. \begin{array}{l} \text{for } Z_L = jX_L \\ \text{purely reactive load} \end{array} \right\} \left. \begin{array}{l} \text{for } Z_L = 0 \\ \text{S.C.} \end{array} \right\} \left. \begin{array}{l} \text{for } Z_L = \infty \\ \text{O.C.} \end{array} \right\}$$

$$Z_L = Z_0 \Rightarrow \Gamma_L = 0$$

$$S = \frac{1 + |\Gamma_L|}{1 - |\Gamma_L|} = 1$$

$$|\Gamma_L| = \sqrt{\frac{jX_L - Z_0}{jX_L + Z_0}} = 1$$

$$\theta_L \neq 0$$

$$\Gamma_L = |\Gamma_L| \cdot e^{j\theta_L}$$

Standing wave pattern

- 1) δ_{\min} depends on the value of Z_L
- 2 a) two successive voltage min $\frac{\lambda}{2}$
- 2 b) min - max $\frac{\lambda}{4}$
- 3) $(V_{\max}, I_{\max}) (V_{\min}, I_{\max}) \rightarrow$ Current and Voltage patterns one shifted by $\frac{\lambda}{4}$ with respect to each other.
- 4 a) Impedance should be purely resistive and becomes maximum.

$$\frac{V_{\max}}{I_{\min}} \triangleq R_{\max} = \frac{|V^+| + |V^-|}{\frac{1}{Z_0}(|V_+| - |V_-|)} = \underline{\underline{Z_0 \cdot S = R_{\max}}}$$

Impedance should be purely resistive and becomes minimum

$$\frac{V_{\min}}{I_{\max}} \triangleq R_{\min} = \frac{|V^+| - |V^-|}{\frac{1}{Z_0}(|V_+| + |V_-|)} = \underline{\underline{\frac{Z_0}{S} = R_{\min}}} \quad R_{\min} \cdot S = Z_0$$

$$i) Z_L = Z_0 \cdot \frac{1 + |P_L|}{1 - |P_L|} \Rightarrow i) S = \frac{1 + |P_L|}{1 - |P_L|} \Rightarrow S = \frac{1 + |P_L|}{1 - |P_L|}$$

$$\frac{\text{reflected}}{\text{incident}} = \frac{V_L^- \cdot e^{-j\beta d}}{V_L^+ \cdot e^{j\beta d}} = P_L \cdot e^{-j2\beta d} = |P_L| \cdot e^{j\theta_L} \cdot e^{-j2\beta d}$$


$$= |P_L| \cdot e^{j(\theta_L - 2\beta d)}$$

θ_L : phase angle of reflection coefficient

At $d = d_{\min}$ \Rightarrow position of V_{\min}

$$\theta_L - 2\beta d_{\min} = -\pi \quad \theta_L = 2\beta d_{\min} - \pi$$

Power Transfer

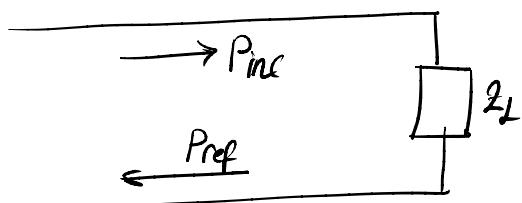

P_L : Power delivered to the load

$$P_{av} = \frac{1}{2} \operatorname{Re}\{V \cdot I^*\}$$

$$P_{inc} = \frac{1}{2} \frac{|V'|^2}{Z_0} \rightarrow \text{real}$$

$$P_{ref} = |P_L|^2 \cdot P_{inc}$$

$$P_L = P_{inc} - P_{ref} = (1 - |P_L|^2) \cdot P_{inc}$$

$$\frac{P_L}{P_{inc}} = 1 - |P_L|^2 \quad \nearrow P_L = 1 \rightarrow \begin{matrix} \text{o.c} \\ \text{s.c} \\ jX_c \end{matrix}$$

Determination of Attenuation Constant

$$\alpha = \operatorname{Re}\{g\} = \operatorname{Re}\left\{ \sqrt{(R+jWL)(G+jWC)} \right\}$$

$$P_{av}(z) = \frac{1}{2} \cdot \frac{|V'|^2}{|Z_0|^2} \cdot \operatorname{Re}\{Z_0\} \cdot e^{-2\alpha z}$$

$P(0)$

$$P_{av}(z) = P(0) \cdot e^{-2\alpha z}$$

$$\frac{dP_{av}(z)}{dz} = -2\alpha \cdot \underbrace{P(0)}_{P_{av}(z)} \cdot e^{-2\alpha z}$$

$$\text{Let } P_{\text{loss}}(z) = - \frac{dP_{\text{out}}(z)}{dz} \text{ Watts/m} \Rightarrow -P_{\text{Loss}}(z) = -2\alpha \cdot P_{\text{out}}(z)$$

$$\alpha = \frac{P_{\text{loss}}(z)}{2 \cdot P_{\text{out}}(z)}$$

$$P_{\text{Loss}}(z) = \frac{1}{2} \left\{ R \cdot |I(z)|^2 + G \cdot |N(z)|^2 \right\}$$