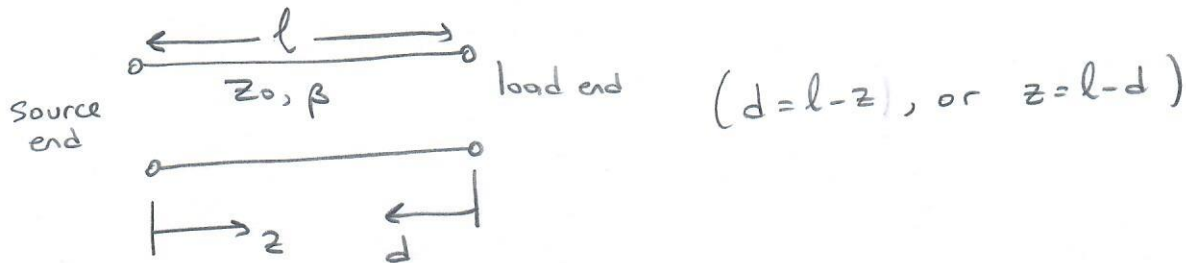


STANDING WAVES in Transmission Lines

Assume lossless T.L. (ie. $R=G=0 \Rightarrow \alpha=0$)
 $\Rightarrow \gamma = j\beta$



$$V(z) = V^+ e^{-j\beta z} + V^- e^{j\beta z} \quad : \text{a standing wave created by oppositely traveling waves.}$$

Or, express it in terms of d (distance measured from load end)

$$V(d) = V_L^+ e^{j\beta d} + V_L^- e^{-j\beta d} \quad \left(\begin{array}{l} \text{Remember; } V_L^+ = V^+ e^{j\beta l} \\ V_L^- = V^- e^{j\beta l} \end{array} \right)$$

$$V(d) = V_L^+ \left(e^{j\beta d} + \frac{V_L^-}{V_L^+} e^{-j\beta d} \right)$$

$$\text{but } \frac{V_L^-}{V_L^+} \triangleq \Gamma_L$$

↓
Load reflection coefficient

$$V(d) = V_L^+ (e^{j\beta d} + \Gamma_L e^{-j\beta d})$$

Standing wave Pattern: plot of $|V(d)|$ versus d
 (which can be measured by a probe moved along the T.L.)

Case 1: Short Circuit Termination (i.e. $Z_L = 0$)

$$\Gamma_L = \frac{Z_L - Z_0}{Z_L + Z_0} \bigg|_{Z_L=0} = -1 \Rightarrow \boxed{\Gamma_L = -1}$$

$$\Rightarrow V(d) = V_L^+ \underbrace{(e^{j\beta d} + (-1)e^{-j\beta d})}_{2j \sin(\beta d)} = 2j V_L^+ \sin \beta d$$


$$\Rightarrow \boxed{|V(d)| = 2|V_L^+| |\sin \beta d|}$$

$|V(d)|_{\max} = 2|V_L^+| = V_{\max}$
 $|V(d)|_{\min} = 0 = V_{\min}$

Define VSWR: Voltage Standing Wave Ratio $\triangleq S$

as $\boxed{S = \frac{V_{\max}}{V_{\min}}}$

For short-circuit termination: $S = \frac{V_{\max}}{V_{\min}} = \frac{2|V_L^+|}{0} = \infty$

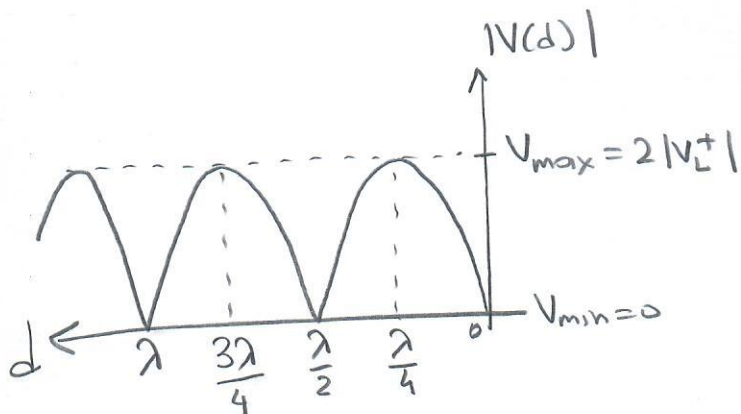

$$\boxed{S = \infty \text{ for } Z_L = 0}$$


Case 2: Open Circuit Termination (i.e. $Z_L = \infty$)

$$\Gamma_L = \frac{Z_L - Z_0}{Z_L + Z_0} \bigg|_{Z_L = \infty} = +1 \Rightarrow \boxed{\Gamma_L = +1}$$

$$\Rightarrow V(d) = V_L^+ \underbrace{(e^{j\beta d} + (1)e^{-j\beta d})}_{2 \cos(\beta d)} = 2V_L^+ \cos \beta d$$

$$\Rightarrow \boxed{|V(d)| = 2|V_L^+| |\cos \beta d|}$$

$\nearrow |V(d)|_{\max} = V_{\max} = 2|V_L^+|$
 $\searrow |V(d)|_{\min} = V_{\min} = 0$

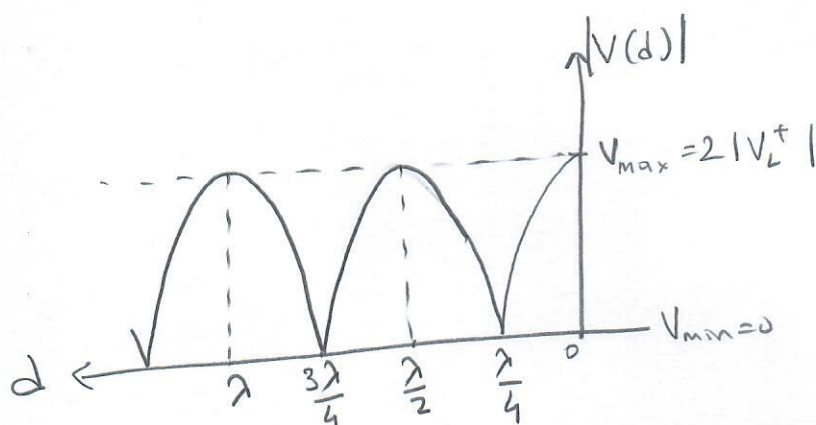

$$S = \frac{V_{\max}}{V_{\min}} = \frac{2|V_L^+|}{0} = \infty$$

$$\boxed{S = \infty \text{ for } Z_L = \infty}$$

Case 3: Arbitrary load impedance Z_L

$$\Gamma_L = \frac{Z_L - Z_0}{Z_L + Z_0} = |\Gamma_L| e^{j\theta_L} \quad \text{where } |\Gamma_L| < 1$$

$$V(d) = V_L^+ e^{j\beta d} + V_L^- e^{-j\beta d}$$

Note that

$$\left\{ \begin{array}{l} |V_L^+| = |V^+ e^{-\alpha \ell}| = |V^+| e^{-\alpha \ell} = |V^+| |e^{-\alpha \ell}| = |V^+| e^{-\alpha \ell} \quad \text{for a lossy TL} \\ \text{but if the TL is lossless, i.e. } \alpha = 0, \Rightarrow |V_L^+| = |V^+| \end{array} \right\} \text{ for lossless TL.}$$

Similarly, $|V_L^-| = |V^-|$

(TL-30)

V_{\max} occurs at those positions along the TL where forward and backward waves are in phase

$$\Rightarrow \boxed{V_{\max} = |V^+| + |V^-|}$$

V_{\min} occurs at those positions along the TL where forward and backward waves are 180° out of phase.

$$\Rightarrow \boxed{V_{\min} = |V^+| - |V^-|}$$

$$S = \frac{V_{\max}}{V_{\min}} = \frac{|V^+| + |V^-|}{|V^+| - |V^-|} \quad \left(\begin{array}{l} \text{divide num. and denom.} \\ \text{by } |V^+| \end{array} \right)$$

$$S = \frac{1 + \frac{|V^-|}{|V^+|}}{1 - \frac{|V^-|}{|V^+|}}$$

where $\Gamma = \frac{V^-}{V^+} \Rightarrow |\Gamma| = \frac{|V^-|}{|V^+|}$
at a given position d .

$$\Rightarrow S = \frac{1 + |\Gamma|}{1 - |\Gamma|}$$

(Note that $\Gamma(d) = \Gamma_L e^{-2\gamma d}$ for a general lossy line with $\gamma = \alpha + j\beta$.)

$$|\Gamma(d)| = |\Gamma_L| |e^{-2\alpha d}| |e^{-2j\beta d}|$$

$$|\Gamma(d)| = |\Gamma_L| e^{-2\alpha d} \quad \text{for a lossy TL}$$

$$\boxed{S = \frac{1 + |\Gamma_L|}{1 - |\Gamma_L|}}$$

in a lossless TL.

$$\boxed{|\Gamma(d)| = |\Gamma_L| \text{ if } \alpha = 0 \text{ in a lossless TL}}$$

Note that the $VSWR \equiv S \geq 1$ always!

$$1 \leq S < \infty$$

happens for a
matched load

$$\boxed{Z_L = Z_0}$$

for which

$$\Gamma_L = \frac{Z_L - Z_0}{Z_L + Z_0} = 0$$

$$\Rightarrow S = \frac{1 + |\Gamma_L|}{1 - |\Gamma_L|} = 1$$

happens whenever $|\Gamma_L| = 1$

(complete reflection cases)

$$\text{for } \boxed{Z_L = jX_L}$$

purely reactive
load

$$\Gamma_L = \frac{Z_L - Z_0}{Z_L + Z_0} \Big|_{Z_L = jX_L}$$

$$|\Gamma_L| = \left| \frac{jX_L - Z_0}{jX_L + Z_0} \right| = 1$$

(where $\theta_L \neq 0$
for $\Gamma_L = |\Gamma_L| e^{j\theta_L}$)

$$\text{for } \boxed{Z_L = 0}$$

(S.C.)

$$\Gamma_L = -1$$


$$|\Gamma_L| = 1$$

$$\text{for } \boxed{Z_L = \infty}$$

(O.C.)

$$\Gamma_L = 1$$

$$|\Gamma_L| = 1$$

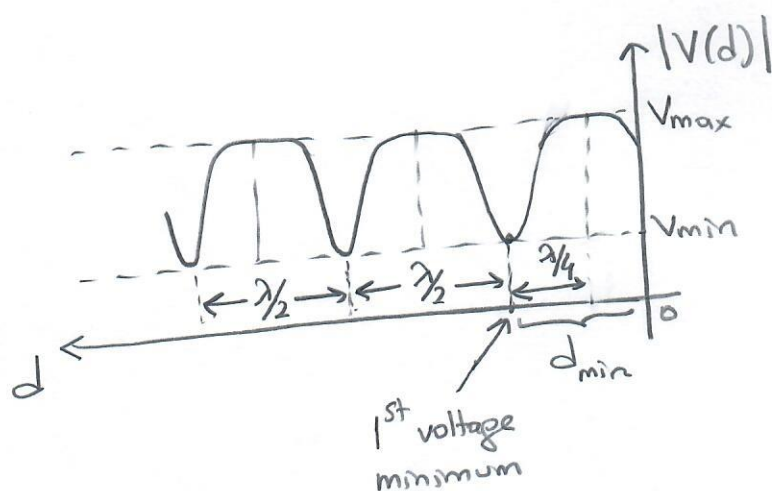

d_{min} : the distance of the
1st voltage minimum
measured from the load.

Note that for an arbitrary
load impedance Z_L , the
voltage standing wave
pattern is periodic
but not necessarily a
sinusoidal plot. Minima
are usually sharper
than maxima, easier to
detect!

Note that in a standing wave pattern:

- 1) d_{\min} depends on the value of load impedance Z_L .
- 2.a) distance between two successive voltage minima is $\frac{\lambda}{2}$.
- 2.b) distance between a voltage minimum and the next voltage maximum is $\frac{\lambda}{4}$.
- 3) At a position where V_{\max} occurs, current is minimum (I_{\min})
 " " " " V_{\min} " , " " maximum (I_{\max})

\Rightarrow Current and voltage patterns are shifted by $\frac{\lambda}{4}$ with respect to each other.

Because:

$$V = V^+ + V^- \quad \left\{ \begin{array}{l} \text{When } V^- \text{ is in phase with } V^+ \\ \text{C.i.e. at a voltage maximum} \end{array} \right.$$

$$I = \frac{1}{Z_0} (V^+ - V^-)$$

$I^- = -\frac{V^-}{Z_0}$ is 180° out of phase
 wrt $I^+ = \frac{V^+}{Z_0}$ (because of (-) sign)

$\Rightarrow I_{\min}$ occurs at locations where V_{\max} occurs, etc.

4.a) At the positions where (V_{\max} and I_{\min}) occur, the impedance of TL is purely resistive and becomes maximum

i.e $\frac{V_{\max}}{I_{\min}} \triangleq R_{\max} = \frac{|V^+| + |V^-|}{\frac{1}{Z_0} (|V^+| - |V^-|)} = Z_0 \frac{|V^+| + |V^-|}{\underbrace{|V^+| - |V^-|}_S} = Z_0 S$

$\Rightarrow \boxed{R_{\max} = Z_0 S}$

4.b) Similarly, at a position where (V_{\min} and I_{\max}) occur, the impedance of the T.L. is purely resistive and becomes minimum.

$$\text{i.e. } \frac{V_{\min}}{I_{\max}} \triangleq R_{\min} = \frac{|V^+| - |V^-|}{\frac{1}{Z_0} (|V^+| + |V^-|)} = \frac{Z_0}{S}$$

$$\boxed{R_{\min} = \frac{Z_0}{S}}$$

Example:

$$\text{Let } Z_L = 50 \, \Omega \text{ and } Z_0 = 75 \, \Omega$$

$$\Gamma_L = \frac{Z_L - Z_0}{Z_L + Z_0} = \frac{50 - 75}{50 + 75} = -0.2 \Rightarrow (|\Gamma_L| = 0.2)$$

$$S = \frac{1 + |\Gamma_L|}{1 - |\Gamma_L|} = \frac{1 + 0.2}{1 - 0.2} = 1.5$$

$$R_{\max} = Z_0 S = 75 \times 1.5 = 112.5 \, \Omega \quad (\text{at } \{V_{\max}, I_{\min}\} \text{ positions})$$

$$R_{\min} = \frac{Z_0}{S} = \frac{75}{1.5} = 50 \, \Omega \quad (\text{at } \{V_{\min}, I_{\max}\} \text{ positions})$$

Note that $R_{\min} = Z_L = 50 \, \Omega$ in this example. As the load impedance is repeated that means we are $n \frac{\lambda}{2}$ (n : an integer) away from the load at $\{V_{\min}, I_{\max}\}$ positions.

Determine the load impedance Z_L

Using the measurements of S and d_{\min}

Assume a lossless T.L. with characteristic impedance Z_0 :

$$Z_L = Z_0 \frac{1 + \Gamma_L}{1 - \Gamma_L} \quad \text{obtained earlier where } \Gamma_L = |\Gamma_L| e^{j\theta_L}$$

Need to find $\begin{matrix} \nearrow |\Gamma_L| \\ \searrow \theta_L \end{matrix}$ to determine the load impedance Z_L .

$$(i) \text{ we know } S = \frac{1 + |\Gamma_L|}{1 - |\Gamma_L|} \Rightarrow \boxed{|\Gamma_L| = \frac{S - 1}{S + 1}}$$

where $S \equiv VSWR$ can be measured.

(ii) A voltage minimum occurs when the reflected (backward) wave is 180° out of phase with the incident (forward) wave.

$$\frac{\text{reflected}}{\text{incident}} = \frac{V_L^- e^{-j\beta d}}{V_L^+ e^{j\beta d}} = \frac{V_L^-}{V_L^+} e^{-j2\beta d} = \underbrace{\Gamma_L}_{|\Gamma_L| e^{j\theta_L}} e^{-j2\beta d}$$


$$= |\Gamma_L| e^{j(\theta_L - 2\beta d)}$$

\Rightarrow At $d = d_{\min}$ (at the position of first voltage minimum)

$$\theta_L - 2\beta d_{\min} = -\pi$$

where d_{\min} can be measured.

$$\Rightarrow \boxed{\theta_L = 2\beta d_{\min} - \pi}$$

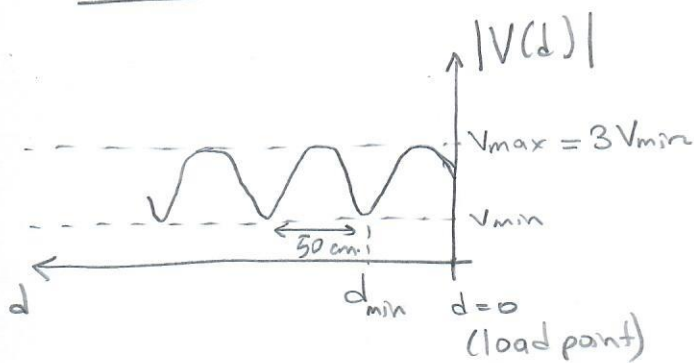Example:

Let $Z_0 = 300(\Omega)$

$$\left. \begin{aligned} d_{\min} &= 30 \text{ cm} \\ \frac{\lambda}{2} &= 50 \text{ cm} \\ S' &= \frac{V_{\max}}{V_{\min}} = 3 \end{aligned} \right\} \text{read from the given standing wave pattern.}$$

$\frac{\lambda}{2} = 50 \text{ cm}$. (distance between two successive minima)

$\Rightarrow \boxed{\lambda = 100 \text{ cm.}} \Rightarrow \beta = \frac{2\pi}{\lambda}$ is known.

$$\theta_L = 2\beta d_{\min} - \pi = 2 \frac{2\pi}{100} 30 - \pi = 0.2\pi \text{ radians}$$

$\boxed{\theta_L = 0.2\pi \text{ rad} = 36^\circ}$


Also, $|\Gamma_L| = \frac{S-1}{S+1} = \frac{3-1}{3+1} = \frac{2}{4} = 0.5 \Rightarrow \boxed{|\Gamma_L| = 0.5}$

$$\Rightarrow Z_L = Z_0 \frac{1 + \Gamma_L}{1 - \Gamma_L} = 300 \frac{1 + 0.5 e^{j0.2\pi}}{1 - 0.5 e^{j0.2\pi}} = \dots$$

$\boxed{Z_L \approx 649 \angle 38^\circ \approx 510 + j400 \Omega}$

↓
Load impedance with an inductive reactance.

Power Transfer by a Transmission Line

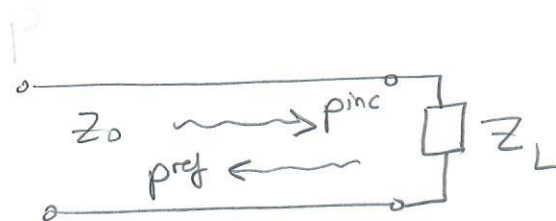

P_L : Power delivered to the load.

$$P_{av} = \frac{1}{2} \operatorname{Re} \{ V I^* \} = \frac{1}{2} \operatorname{Re} \{ V^2 / Z \}$$

$$\left\{ \begin{array}{l} p^{inc} = \frac{1}{2} \frac{|V^+|^2}{Z_0} \quad (\text{assuming } Z_0 \text{ is real}) \\ p^{ref} = |\Gamma_L|^2 p^{inc} \end{array} \right.$$

$$P_L = p^{inc} - p^{ref} = (1 - |\Gamma_L|^2) p^{inc}$$

$$\text{or } \frac{P_L}{p^{inc}} = 1 - |\Gamma_L|^2$$

Note that $P_L = 0$ for a load

- $\rightarrow Z_L = \infty$ (open ckt)
- $\rightarrow Z_L = 0$ (short ckt)
- $\rightarrow Z_L = jX_L$ (purely reactive)

for which $|\Gamma_L| = 1 \Rightarrow P_L = 0$

Determination of Attenuation Constant (α)

(i) If R, L, G, C and $\omega = 2\pi f$ are known, then

$$\alpha = \operatorname{Re}\{\gamma\} = \operatorname{Re}\left\{\sqrt{(R + j\omega L)(G + j\omega C)}\right\}$$

(ii) α can also be determined based on power relations:

Consider for example, a forward traveling wave along the T.L. with

$$\left. \begin{aligned} V(z) &= V^+ e^{-\alpha z} e^{-j\beta z} \\ I(z) &= \frac{V^+}{Z_0} e^{-\alpha z} e^{-j\beta z} \end{aligned} \right\} \begin{aligned} P_{av}(z) &= \frac{1}{2} \operatorname{Re}\{V(z)I^*(z)\} \\ &\downarrow \\ &\text{Average power} \\ &\text{propagating along the T.L.} \end{aligned}$$

$$\begin{aligned} P_{av}(z) &= \frac{1}{2} \operatorname{Re}\left\{ V^+ e^{-\alpha z} e^{-j\beta z} \frac{(V^+)^*}{Z_0^*} e^{-\alpha z} e^{+j\beta z} \right\} \\ &= \frac{1}{2} \operatorname{Re}\left\{ |V^+|^2 e^{-2\alpha z} \underbrace{\frac{1}{Z_0^*} \frac{Z_0}{Z_0^2}}_{\left(\begin{smallmatrix} \text{divide and} \\ \text{multiply by} \\ Z_0 \end{smallmatrix}\right)} \right\} \end{aligned}$$

$$= \frac{1}{2} \frac{|V^+|^2}{|Z_0|^2} e^{-2\alpha z} \operatorname{Re}\{Z_0\}$$

$$P_{av}(z) = \underbrace{\frac{1}{2} \frac{|V^+|^2}{|Z_0|^2} \operatorname{Re}\{Z_0\}}_{P(0) = \text{power at } z=0} e^{-2\alpha z}$$

$$\Rightarrow \boxed{P_{av}(z) = P(0) e^{-2\alpha z}}$$

$$\Rightarrow \frac{d P_{av}(z)}{dz} = -2\alpha \underbrace{P(0) e^{-2\alpha z}}_{P_{av}(z)}$$

$$\Rightarrow \boxed{\frac{d P_{av}(z)}{dz} = -2\alpha P_{av}}$$

Let $P_{loss}(z) = - \frac{d P_{av}(z)}{dz}$ Watts/m : Time-average power loss per unit length on the T.L -

$$-P_{loss}(z) = -2\alpha P_{av}(z)$$

$$\Rightarrow \boxed{\alpha = \frac{P_{loss}(z)}{2 P_{av}(z)}}$$

where $P_{loss}(z)$ can be obtained from:

$$\boxed{P_{loss}(z) = \frac{1}{2} \left\{ R |I(z)|^2 + G |V(z)|^2 \right\}}$$