

EE303 Recitation 10

- Q1.** A 100 km telephone line has a series resistance of $4 \Omega/\text{km}$, an inductance of $3 \text{ mH}/\text{km}$, a leakage conductance of $1 \mu\text{S}/\text{km}$, and a shunt capacitance of $0.015 \mu\text{F}/\text{km}$, at an angular frequency $\omega = 5000 \text{ rad/s}$. The load at the receiving end consists of a 200Ω resistor and the load current is $I_L = -0.115 + j0.0268 \text{ A}$.
- Find the voltage and current as functions of z (the distance from the load), and calculate their values at the midpoint of the line.
 - At the sending end there is a generator operating at 5000 radians per second, in series with a resistance of 300Ω . Determine the generator voltage.

Solution:

From the given parameters of the transmission line we can calculate the characteristic impedance as

$$\begin{aligned} Z_0 &= \sqrt{\frac{R + j\omega L}{G + j\omega C}} = \sqrt{\frac{4 + j5000 \times 3 \times 10^{-3}}{10^{-6} + j5000 \times 0.015 \times 10^{-6}}} = 10^3 \sqrt{\frac{4 + j15}{1 + j75}} \\ &= 10^3 \sqrt{\frac{15.52 \angle 75^\circ}{75 \angle 89.2^\circ}} = 454.9 \angle -7.1^\circ \approx 451.5 - j56.1 \Omega \end{aligned}$$

and the propagation factor as

$$\begin{aligned} \gamma &= \sqrt{(R + j\omega L)(G + j\omega C)} = 10^{-3} \sqrt{(4 + j15)(1 + j75)} \\ &= 10^{-3} \sqrt{(15.52 \angle 75^\circ)(75 \angle 89.2^\circ)} = 34.1 \angle 82.1^\circ \\ &= (4.66 + j33.8) \times 10^{-3} \end{aligned}$$

The voltage and current waves at the load end must satisfy

$$\begin{aligned} V(z=0) &= [V_0^+ e^{-\gamma z} + V_0^- e^{\gamma z}]_{z=0} = V_0^+ + V_0^- = Z_L I_L \\ I(z=0) &= \left[\frac{V_0^+}{Z_0} e^{-\gamma z} - \frac{V_0^-}{Z_0} e^{\gamma z} \right]_{z=0} = \frac{V_0^+ - V_0^-}{Z_0} = I_L \end{aligned}$$

and we know the values of Z_L and I_L . We can solve for V_0^+ and V_0^- to get

$$\begin{aligned} V_0^+ + V_0^- &= 200(-0.115 + j0.0268) \\ V_0^+ - V_0^- &= (451.5 - j56.1)(-0.115 + j0.0268) \\ V_0^+ &= -36.7 + j11.9 \text{ V}; \quad V_0^- = 13.7 - j6.6 \text{ V} \end{aligned}$$

- The voltage and current waves are now easy to write by direct substitution. At the midpoint of the line ($z = -50 \text{ km}$) we have

$$\begin{aligned} \gamma z &= (4.66 + j33.8) \times 10^{-3} \times (-50) = -0.23 - j1.69 \\ V(z = -50 \text{ km}) &= (-36.7 + j11.9)e^{-(0.23 - j1.69)} + (13.7 - j6.6)e^{(0.23 - j1.69)} \\ &= -15.9 - j57.8 \text{ V} \\ I(z = -50 \text{ km}) &= \frac{-36.7 + j11.9}{451.5 - j56.1} e^{-(0.23 - j1.69)} - \frac{13.7 - j6.6}{451.5 - j56.1} e^{(0.23 - j1.69)} \\ &= -3.6 - j82.5 \text{ mA} \end{aligned}$$

- At the generator end the line voltage and current can be found as follows:

$$\gamma z = (4.66 + j33.8) \times 10^{-3} \times (-100) = -0.46 - j3.38$$

$$V(z = -100 \text{ km}) = (-36.7 + j11.9)e^{-(0.46-j3.38)} + (13.7 - j6.6)e^{-(0.46-j3.38)}$$

$$= 53.5 + j1.4 \text{ V}$$

$$I(z = -100 \text{ km}) = \frac{-36.7 + j11.9}{451.5 - j56.1}e^{-(0.46-j3.38)} - \frac{13.7 - j6.6}{451.5 - j56.1}e^{-(0.46-j3.38)}$$

$$= 152.1 - j5.1 \text{ mA}$$

which means that the generator side sees an impedance of

$$Z_{in} = \frac{V(z = 100 \text{ km})}{I(z = 100 \text{ km})} = \frac{53.5 + j1.4}{152.1 - j5.1} \approx 350 \Omega$$

The generator voltage can then be determined from the following equation:

$$V(z = 100 \text{ km}) \approx \frac{350}{350 + 300}V_G$$

$$V_G \approx 53.5 \times \frac{13}{6} \approx 116 \text{ V}.$$

Q2. A transmission line operating at 125 MHz has the characteristics $Z_0 = 40 \Omega$, $\alpha = 0.173$ dB/m, and $\beta = 0.75$ rad/m. Find the line parameters R , L , G , and C .

Solution:

In a distance of 1 m, the voltage is scaled by $-\alpha = -0.173$ dB or by a factor of $10^{-0.173/20} = 0.98$. This ratio must be $e^{-\alpha_{\text{Np}}}$, thus the attenuation constant is $\alpha = 0.02$ Np/m. Since Z_0 is real, the line is distortionless, i.e.,

$$R + j\omega L = k(G + j\omega C)$$

for some real k . Equating the real and imaginary parts we get

$$k = \frac{R}{G} = \frac{j\omega L}{j\omega C}$$

If we substitute $R = LG/C$ into the expression for Z_0 , we get

$$Z_0 = \sqrt{\frac{R + j\omega L}{G + j\omega C}} = \sqrt{\frac{LG/C + j\omega L}{G + j\omega C}} = \sqrt{\frac{L}{C}} \sqrt{\frac{G + j\omega C}{G + j\omega C}} = \sqrt{\frac{L}{C}} \Rightarrow \sqrt{L} = 40\sqrt{C}$$

Now, if we substitute $R = LG/C$ into the expression for the propagation factor, we get

$$\alpha + j\beta = \sqrt{(R + j\omega L)(G + j\omega C)} = \sqrt{(LG/C + j\omega L)(G + j\omega C)}$$

$$= \sqrt{L/C(G + j\omega C)(G + j\omega C)} = \sqrt{\frac{L}{C}}(G + j\omega C)$$

Which yields

$$\alpha = G \sqrt{\frac{L}{C}}; \quad \beta = \omega \sqrt{LC}$$

From the equation for β we can find

$$\beta = 2\pi f \sqrt{LC} = 2\pi f \sqrt{L} \sqrt{C} = 2\pi f Z_0 C \Rightarrow$$

$$C = \frac{\beta}{2\pi f Z_0} = \frac{0.75}{2 \times 125 \times 10^6 \times 40 \times \pi} = 23.9 \text{ pF/m}$$

$$L = Z_0^2 C = 38.2 \text{ nH/m}$$

From $\alpha = G \sqrt{L/C}$ and $RC = LG$, we find

$$G = 0.5 \text{ mS/m} \quad \text{and} \quad R = \alpha Z_0 = 0.8 \Omega/\text{m}.$$

Q3. Consider a lossless transmission line having distributed parameters $L = 245 \text{ nH/m}$ and $C = 200 \text{ pF/m}$. The line is terminated with a resistor $R_L = 100 \Omega$. The operating frequency is $f = 1 \text{ GHz}$.

- Determine the characteristic impedance and phase velocity of the line.
- Determine the input impedance seen looking into the input terminals of the line at 1 GHz , if the length of the line is 35.7 mm .
- Determine the VSWR of the load.

Solution:

- For a lossless transmission line the characteristic impedance is given by

$$Z_0 = \sqrt{\frac{L}{C}} = \sqrt{\frac{245 \times 10^{-9}}{200 \times 10^{-12}}} = 35 \Omega$$

$$\beta = \text{Im}(\gamma) = \omega\sqrt{LC} = 2\pi \times 10^9 \sqrt{245 \times 10^{-9} \times 200 \times 10^{-12}} = 44 \text{ rad/m}$$

$$v_p = \frac{\omega}{\beta} = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{245 \times 10^{-9} \times 200 \times 10^{-12}}} = 1.429 \times 10^8 \text{ m/s}$$

- The input impedance is given by

$$Z_{in} = Z_0 \frac{Z_L + jZ_0 \tan(\beta l)}{Z_0 + jZ_L \tan(\beta l)}$$

Using the numerical values $Z_L = 100 \Omega$, $Z_0 = 35 \Omega$, and $\beta l = 44 \times 0.0357 = \pi/2$. The value of $\tan(\beta l)$ goes to infinity and in the limit we have

$$Z_{in} = \frac{Z_0^2}{Z_L} = \frac{35^2}{100} = 12.25 \Omega$$

- The voltage standing wave ratio (VSWR) is the value of the maximum magnitude of the voltage wave to its minimum value, which is

$$s = \frac{|V_0^+ + V_0^-|}{|V_0^+ - V_0^-|} = \frac{1 + \left|\frac{V_0^-}{V_0^+}\right|}{1 - \left|\frac{V_0^-}{V_0^+}\right|}$$

where $|V_0^-/V_0^+|$ is the reflection coefficient. At the load end we have

$$V_0^+ + V_0^- = R_L I_L$$

$$V_0^+ - V_0^- = Z_0 I_L$$

which gives

$$\frac{V_0^-}{V_0^+} = \Gamma = \frac{R_L - Z_0}{R_L + Z_0} = \frac{100 - 35}{100 + 35} = 0.481$$

and

$$s = \frac{20}{7} = 2.857$$